Warmup

Use a k-map to find a minimal implementation of this truth table:

Α	В	С	D	Y	A B C D Y		A	B	
0	0	0	0	. 0	10000	00		l	10
0	0	0	1	Θ	1001 1	00 C	> 0	0	υ
0	0	1	0	1	10100	01		6	1
0	0	1	1	1	1011 1	CD T		<u> </u>	
0	1	0	0	Θ	1 1 0 0 0	ι ι 1	I	1	1
0	1	0	1	Θ	1 1 0 1 1	10	1	٥	0
0	1	1	0	1	1 1 1 0 0	ا لـ		J	
0	1	1	1	1	1 1 1 1 1	ĀC	+ 1	1 D	

EE 201: Multiplexers and FPGAs

Steven Bell 30 January 2024



By the end of class today, you should be able to:

- Explain what a multiplexer is
- Draw a logic diagram using a 2^N-input multiplexer to implement an N-variable boolean equation
- Describe the basic structure of an FPGA

Both [multiplexers and decoders] seem like obscure ways to implement things we already have. Why use them?

Some schematic terminology



What is a multiplexer?



bricklink.com/v2/catalog/catalogitem.page?P=2859#T=C



bricklink.com/v2/catalog/catalogitem.page?P=2859#T=C



More than 4:1?

If we have N select lines, we can choose from 2^{N} inputs:



What good are multiplexers?

1) Allow you to select one signal out of many



$$if (case 1)$$

$$y = 5$$

else if (case 2)

$$y = 8$$

else

$$y = 0$$



What good are multiplexers?

1) Allow you to select one signal out of many

1B) Allow you to make a choice based on a control value

It's like an **if** or **case** statement in software

Another multiplexer example

1B) Like an **if** statement in hardware



And back in the old days...

1) Allow you to select one signal out of many

1B) Allow you to make a choice based on a control value

It's like an **if** or **case** statement in software

2) Make it easy to implement arbitrary logic functions

Implementing XOR

Using a mux to implement a logic function



Look-up tables (LUTs)

A look-up-table is basically a mux where the inputs are little memory boxes statically configured to be 0 or 1.



Look-up table practice

Use a 3-input LUT to implement $A \oplus B \oplus C$



Look-up table practice

Use a 3-input LUT to implement a 2:1 multiplexer



Introducing FPGAs

An FPGA is like a big chip full of logic gates that can be wired together by "programming" it.

iCE40UP block diagram

Clock stuff **Fixed-function** multipliers Memory Logic "fabric"

Fixed-function I/O modules



Figure 3.1. iCE40UP5K Device, Top View

iCE40UP logic element



Shared Block-Level Controls

Figure 3.2. PLB Block Diagram

A better definition

An FPGA is a chip full of configurable **look-up-tables** with configurable **interconnections** and storage.

Decoders

Take a binary number as an input, and set the corresponding output high.



Building a decoder $\Rightarrow \Rightarrow \Rightarrow = 2$



Building a decoder with fewer transistors



What could you use a decoder for?

You have a whole bunch of things to activate one at a time (say, memory cells)



For Thursday

1. Read the book (2.9) and complete the reading check