

EE 201: More sequential logic in SystemVerilog

Steven Bell

27 February 2024




By the end of class today, you should be able to:

- Build a design for an FPGA from HDL to bitstream
- Build slightly more complicated sequential circuits using SystemVerilog

Blinking an LED?

$\sim 1\text{ Hz}$

 
Design a circuit to blink an LED at a rate humans can see.
Assume your input clock runs at 48MHz.



$$1\text{ MHz} = 10^6 \approx 2^{20}$$

$\Rightarrow 26 \text{ flip-flops}$

PWM controller

 

Loadable counter

FPGA toolchains

See link on course website

For Thursday

1. Read book (3.4, 4.6)
2. Complete HW 3 if you haven't