
 


Warmup



Draw a state diagram for the circuit below:

 If it helps, assume that both FFs are 0, and work from there



Warmup

What about this circuit?

  

EE 201: State machines, part 2

Steven Bell


5 March 2024

Logistics



- Exam is March 14 (Thursday before break)
Review materials up after class!
- Paper HW 2 is due Thursday, solutions are online

Mealy vs Moore (See also Harris example 3.7)

Moore

 

Mealy

  

When is this read
by a downstream FF?

FSMs in SystemVerilog

Design a circuit which sets a flag high when the "data" input has been high for 3 clock cycles. The flag should stay high until the reset signal is asserted (i.e., = 1)

