

# Welcome back!

Please fill out a name tent with whatever you want us to call you.



# EN 1-24: Engineering in the Kitchen

Steven Bell

14 September 2020



# Quick review of last time

Is it possible to have a voltage without a current?

Respond at [pollev.com/stevenbell](https://pollev.com/stevenbell)

# Quick review of last time

Is it possible to have a voltage without a current?

Is it possible to have a current without a voltage?

Respond at [pollev.com/stevenbell](https://pollev.com/stevenbell)

# By the end of class today, you should be able to:

- Explain what resistance is
- Use Ohm's law to calculate  $V/I/R$
- Explain what power is, and how it's different from energy
- Use Watt's law to calculate power

# Marble-track resistor



From the fantastic engineering/woodworking site [woodgears.ca](http://woodgears.ca)

# Ohm's Law

For a resistor (and only a resistor):

$$I = \frac{V}{R}$$

**R** is the resistance, measured in Ohms

Represented with the schematic symbol:



# WARNING WARNING WARNING!

Not everything behaves like a resistor.

For example:

- Diodes (and light-emitting diodes, LEDs)


- Capacitors and inductors, which store energy

- Batteries

Don't just blindly apply Ohm's law!



What is the current  $i$ ?

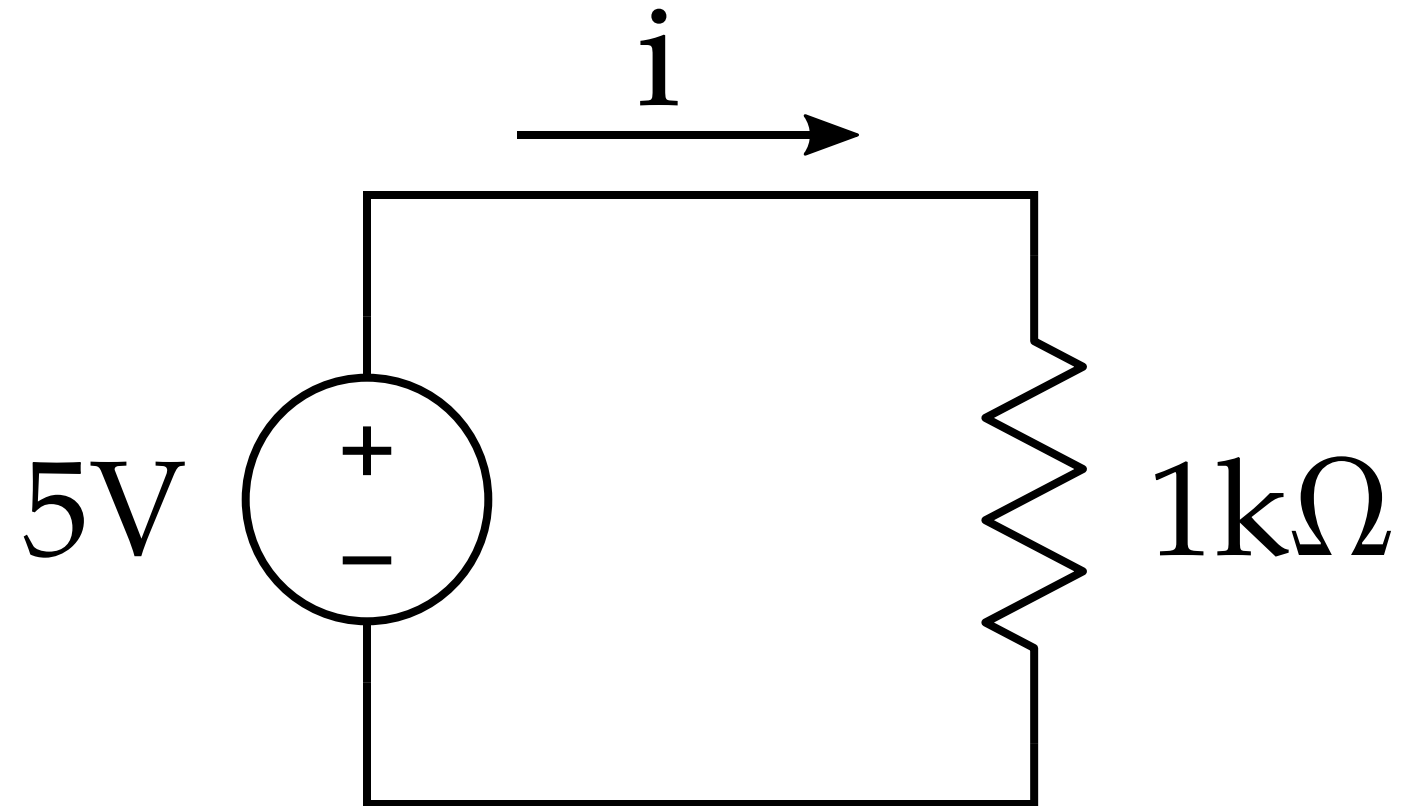


**Let's measure some more interesting things.**
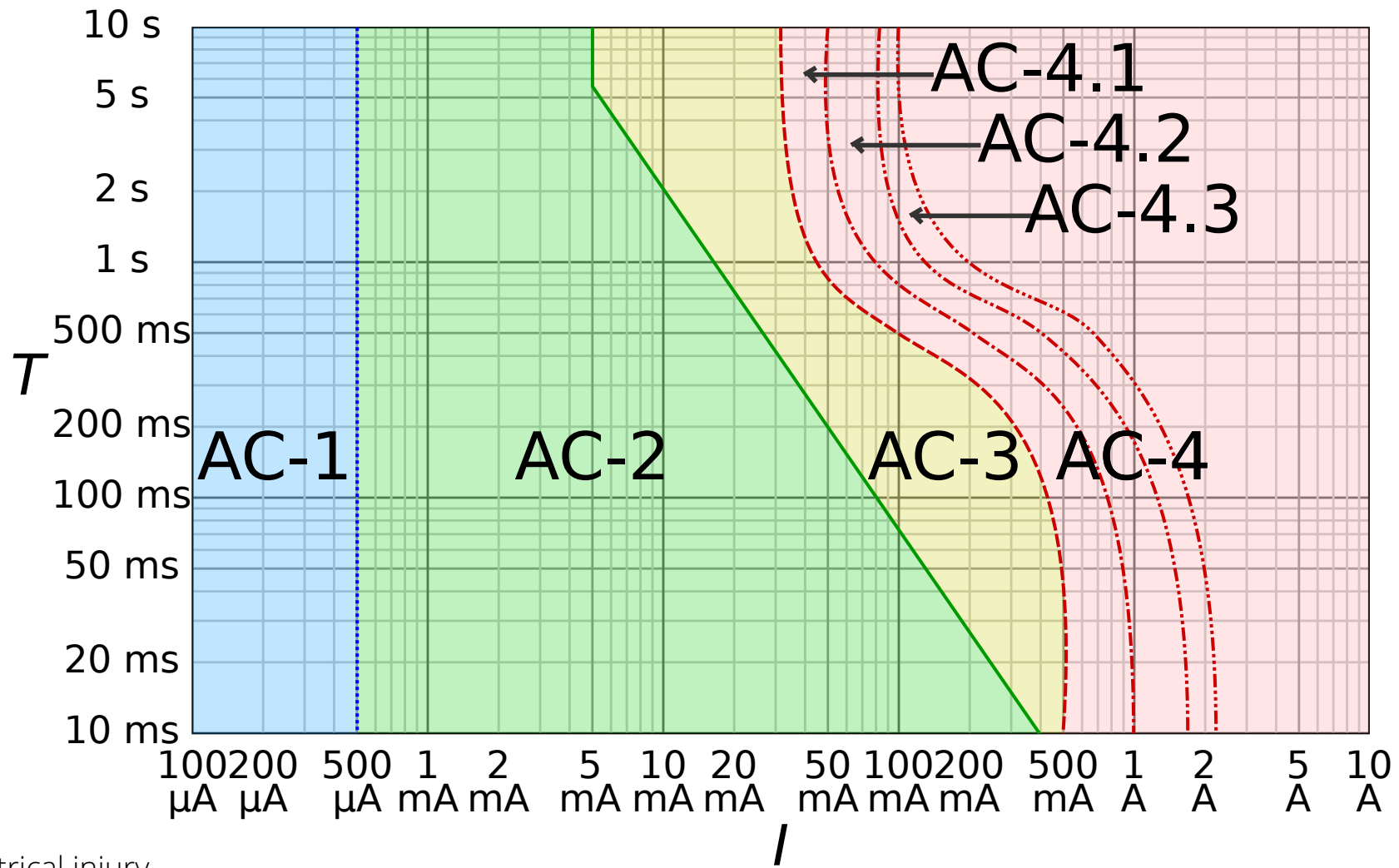
# Let's talk about safety

Electricity can kill you. [citation needed]

But how? And is it the voltage or current that's dangerous?



# Ok, so what *voltage* is dangerous?

A phone charges at 1A or more, so why isn't that dangerous? (Or is it?)

# Intermission: Interview your partner

I'll be coming around to take pictures

# Intermission: Interview your partner


Who is from the furthest away?

Who has the largest / most interesting pet?

Who has the most siblings?

Who has an interesting hobby?

# Collecting energy from marbles

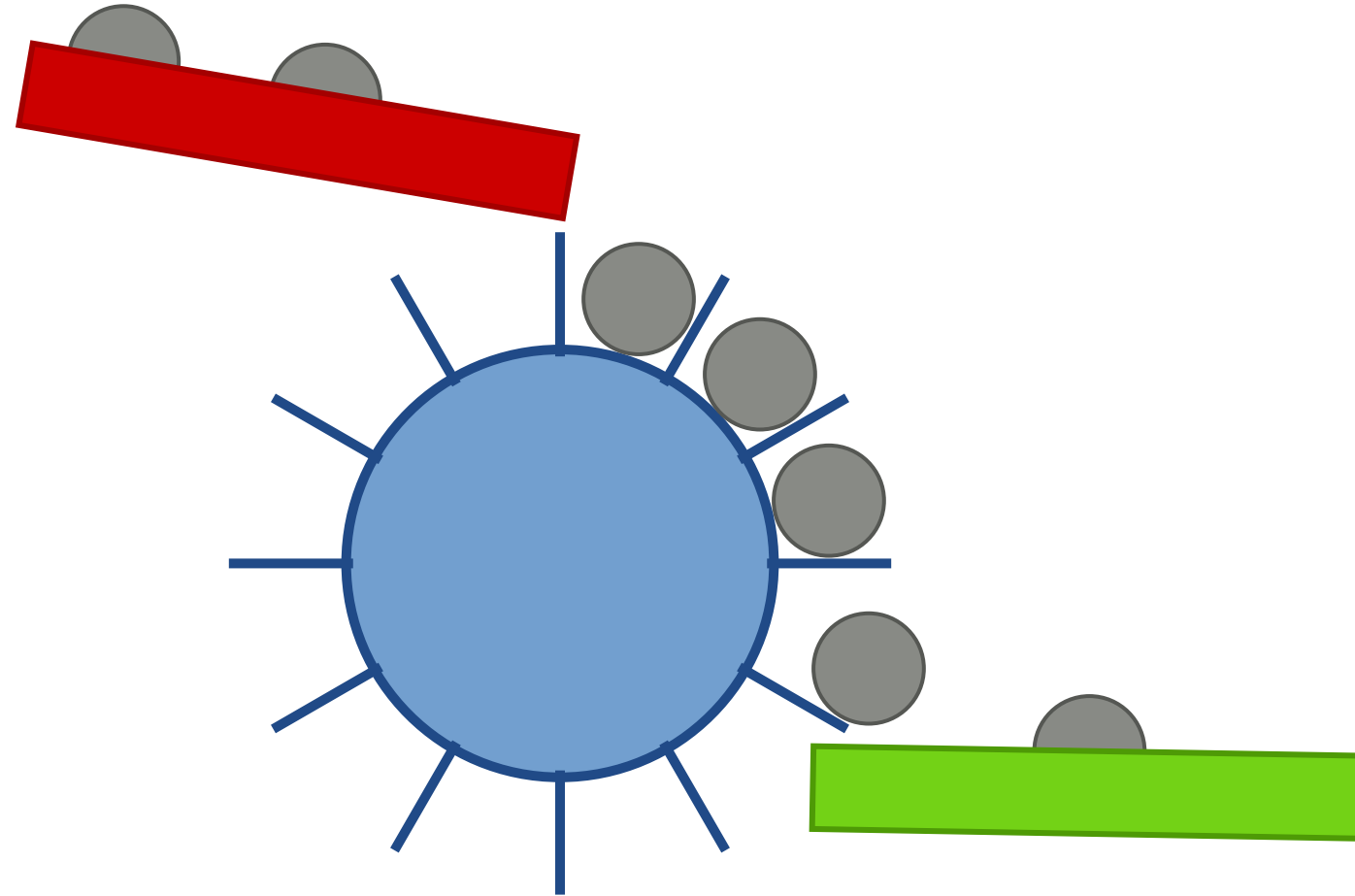

What determines how much energy I get?



$$V = \frac{\text{Joules}}{\text{Coulomb}} \quad I = \frac{\text{Coulombs}}{\text{second}}$$


$$V \cdot I = \frac{\text{Joules}}{\text{Coulomb}} \frac{\text{Coulombs}}{\text{second}} = \frac{\text{Joules}}{\text{second}}$$

Joules/sec is called a **Watt**, abbreviated **W**.

How much power does a light bulb use, if it is connected to 120V and draws 0.5 A?

**A more exciting example**

# Why does the light bulb light up?

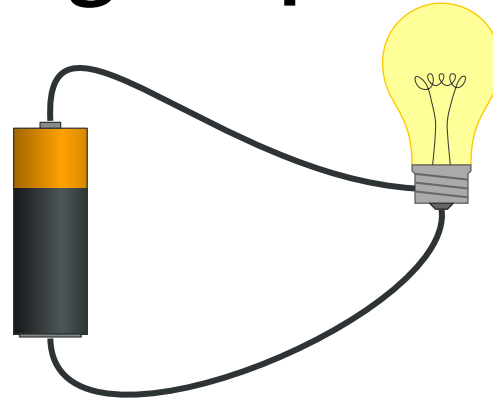

The filament gets hot and glows because:

- A)** the current is used up in the light bulb, becoming heat.
- B)** the voltage accelerates electrons and they collide with the metal, losing their energy as heat.
- C)** charges pile up inside the filament, and the repulsion of their electric fields creates heat.
- D)** this is a trick question; the light bulb doesn't light up.

# Bonus material: Alternating current

# Wrapping up

PollEverywhere: what is one question you have after today's class?