

Warmup

Is it possible to have a voltage without a current?

Respond at pollev.com/stevenbell

Warmup

Is it possible to have a voltage without a current?

Is it possible to have a current without a voltage?

Respond at pollev.com/stevenbell

Circuits

charge

electric field

electrical potential
energy

voltage

current
(charge/second)

Marble machine

mass

gravity

potential
energy

height

marbles/second

Spintronics

chain tension

chain speed
(links/second)

EN 1: Engineering in the Kitchen

Steven Bell

11 September 2023

By the end of class today, you should be able to:

- Explain what resistance is, and measure it with your DMM
- Use Ohm's law to calculate V/I/R
- Explain what power is, and how it's different from energy
- Explain why electricity is dangerous, and under what circumstances
- Use Watt's law to calculate power


Marble-track resistor



From the fantastic engineering/woodworking site woodgears.ca

DC Volts

Resistance
(Ohms Ω)

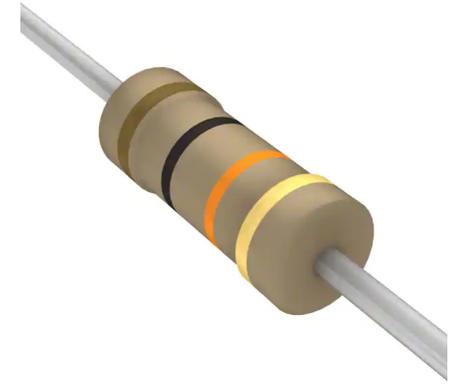


Fixed resistor



Photoresistor

Measuring resistance

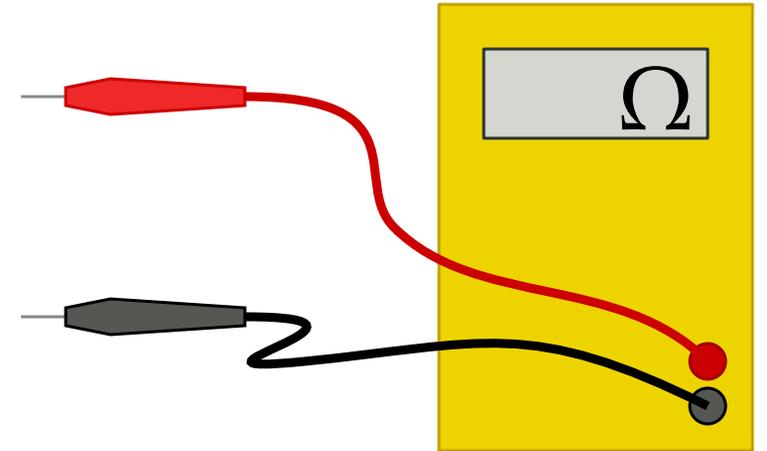- 1) Pick an appropriate resistance scale
- 2) Put the **black** lead on one side
- 3) Put the **red** lead on the other side
- 4) Read the result!



What happens if you use the wrong scale?

What happens if you swap the leads?

Why do you need two leads, anyway?

Ohm's Law

For a resistor (and only a resistor):


$$I = \frac{V}{R}$$

R is the resistance, measured in Ohms

Represented with the schematic symbol:



What is the current i ?

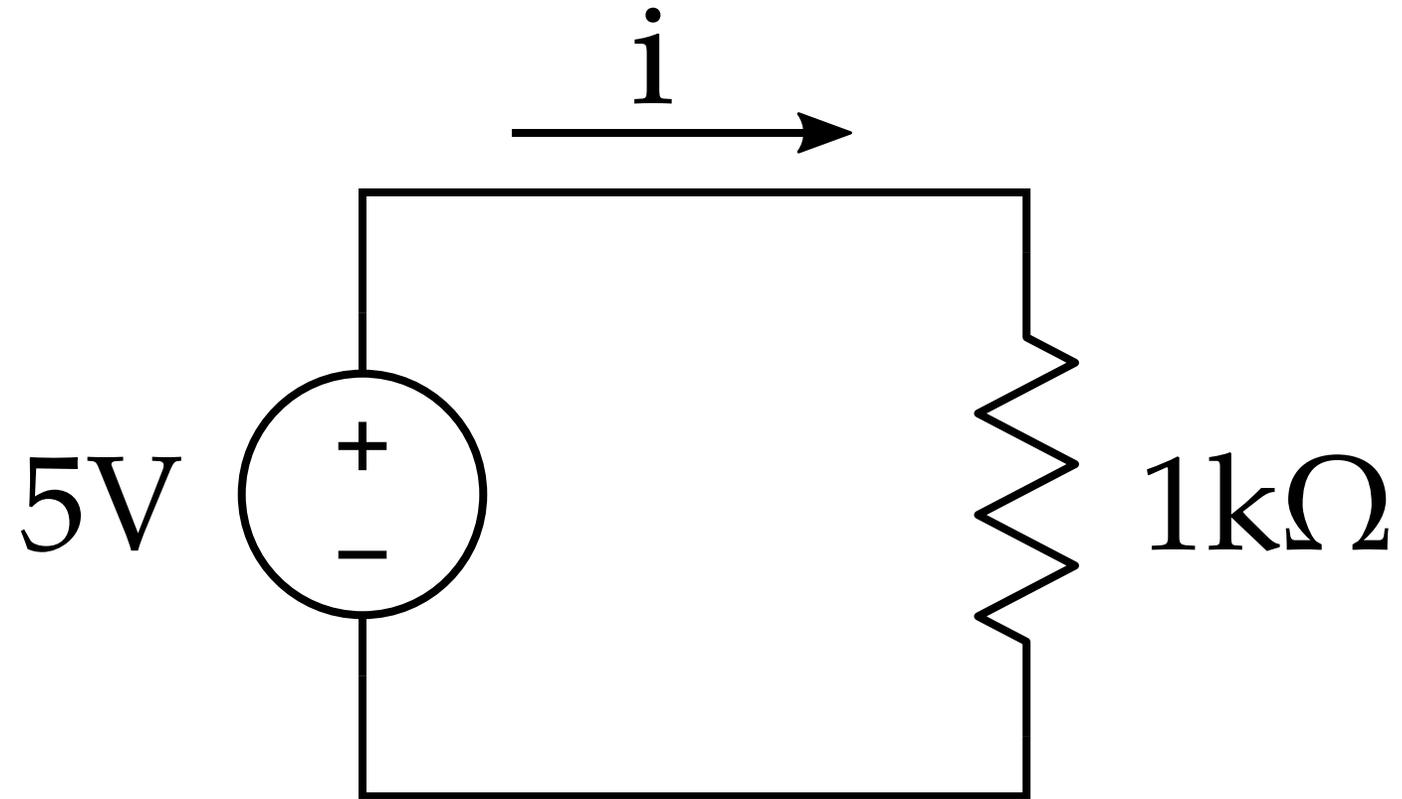

WARNING WARNING WARNING!

Not everything behaves like a resistor.

For example:

Diodes (and light-emitting diodes, LEDs)

Capacitors and inductors, which store energy

Batteries

Don't just blindly apply Ohm's law!

Warmup, part 2

Introduce yourself to someone you haven't met (move around!).

Tell them about something you do often because you love to do it.

Some problems with grades

There are a number of problems with traditional grades

- Grades are the ultimate extrinsic motivator, i.e., they suck all the fun out of learning.
- Adding up assignment scores is a 1-dimensional representation of your learning (at best)

This course has no grades

There will be **zero** graded assignments in this course

Instead:

- Teaching staff will give copious feedback on projects
- There will be self-graded homework exercises
- We'll regularly engage in "metacognitive" excersises
- You and I will agree on your final letter grade by consensus

But what about...?

Many of you depend on numerical and letter grades...

- to know "how well you are doing"

But what about...?

Many of you depend on numerical and letter grades...

- to know "how well you are doing"
- for your sense of self-worth



NOTHING IS A MISTAKE.
THERE'S NO WIN
AND NO FAIL.

THERE'S ONLY

MAKE

JOHN CAGE


Let's talk about safety

Electricity can kill you. [citation needed]

But how? And is it the voltage or current that's dangerous?

StyroPyro explains: [youtube.com/shorts/8Wx6-ysokJU](https://www.youtube.com/shorts/8Wx6-ysokJU)


Effect of electricity on the body

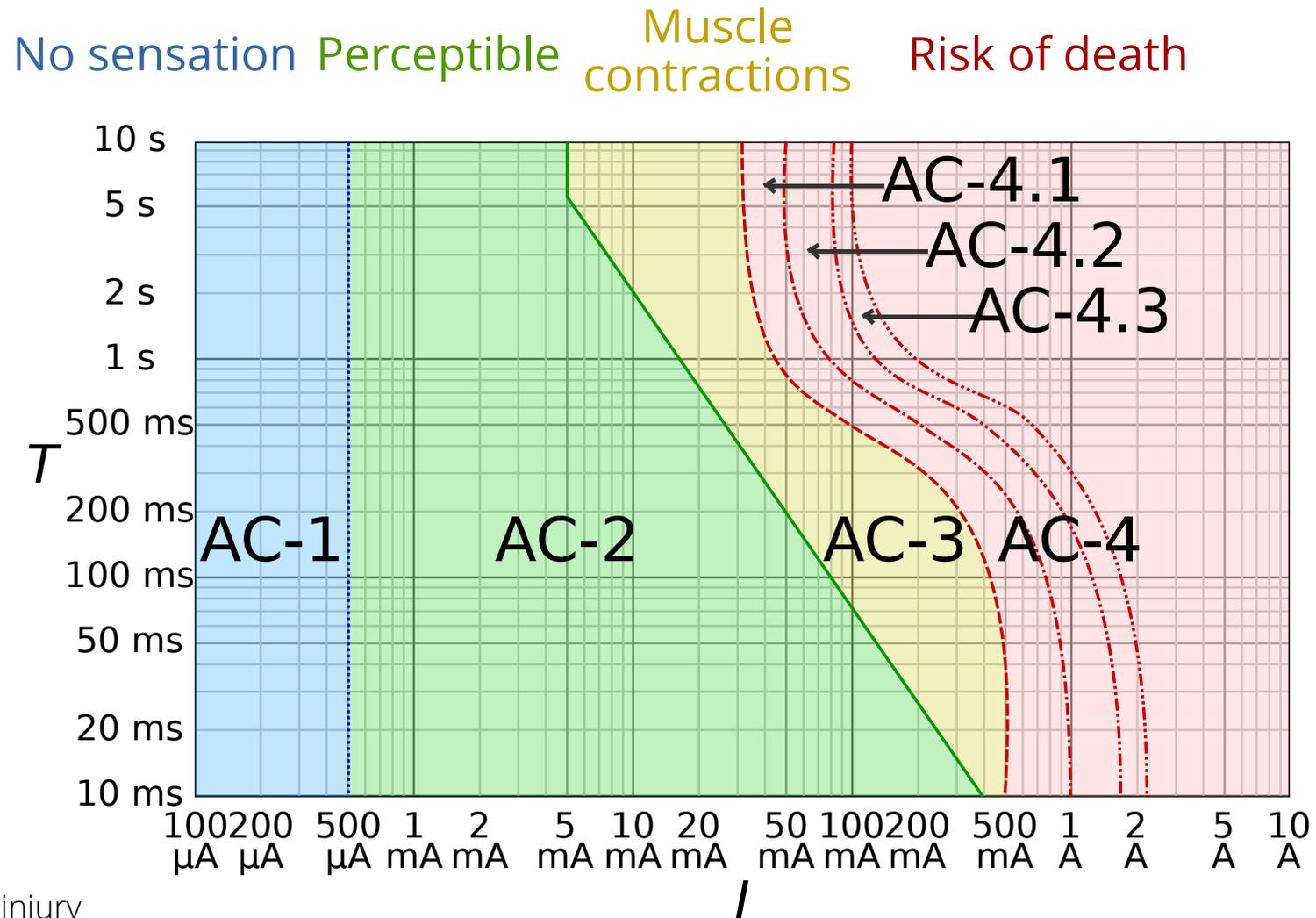

Ok, so what *voltage* is dangerous?

A phone charges at 1A or more, so why isn't that dangerous? (Or is it?)

Collecting energy from marbles

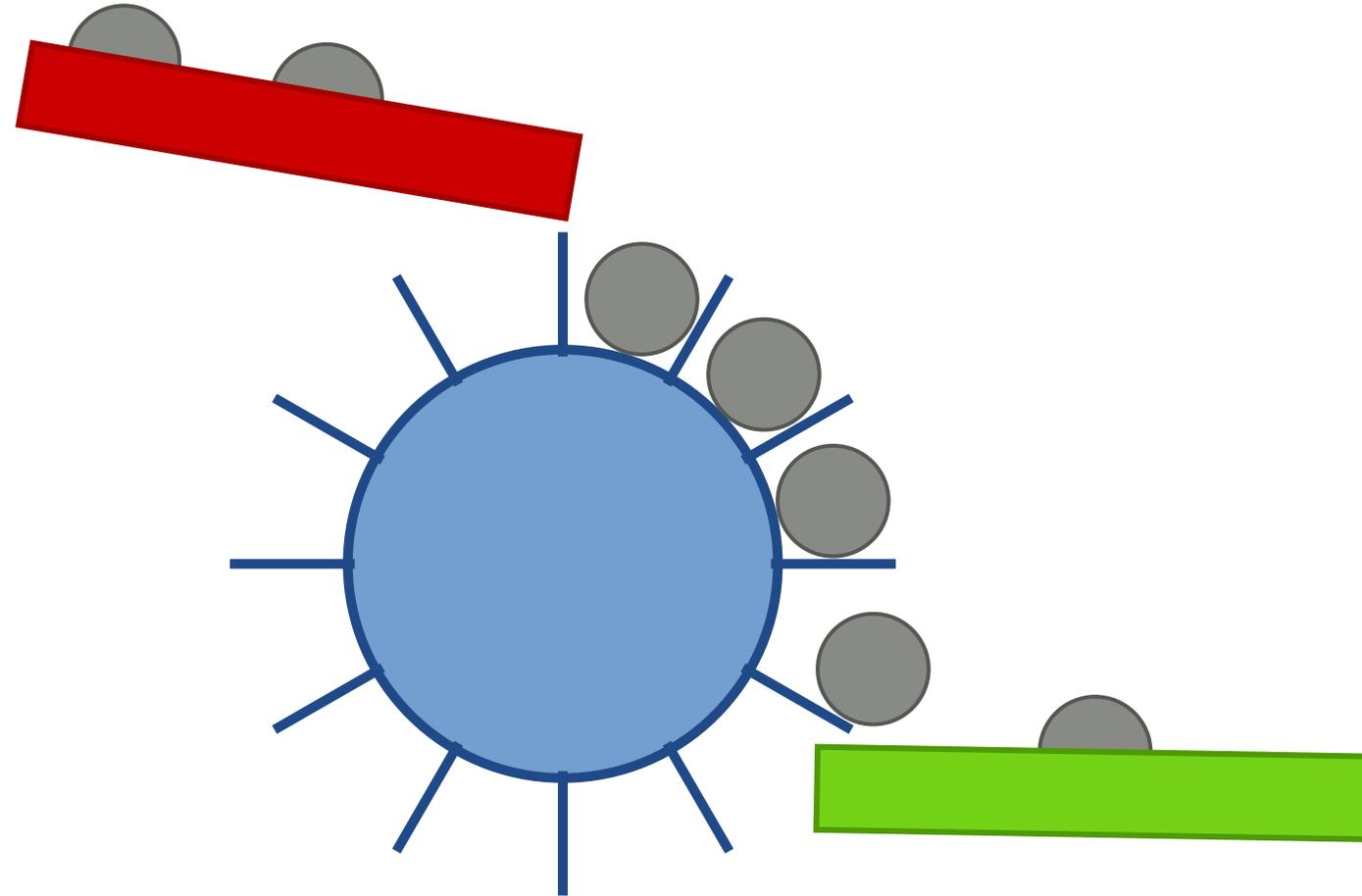

What determines how much energy I get?


$$V = \frac{\text{Joules}}{\text{Coulomb}} \quad I = \frac{\text{Coulombs}}{\text{second}}$$

$$V \cdot I = \frac{\text{Joules}}{\text{Coulomb}} \frac{\text{Coulombs}}{\text{second}} = \frac{\text{Joules}}{\text{second}}$$

Joules/sec is called a **Watt**, abbreviated **W**.

How much power does a light bulb use, if it is connected to 120V and draws 0.5 A?

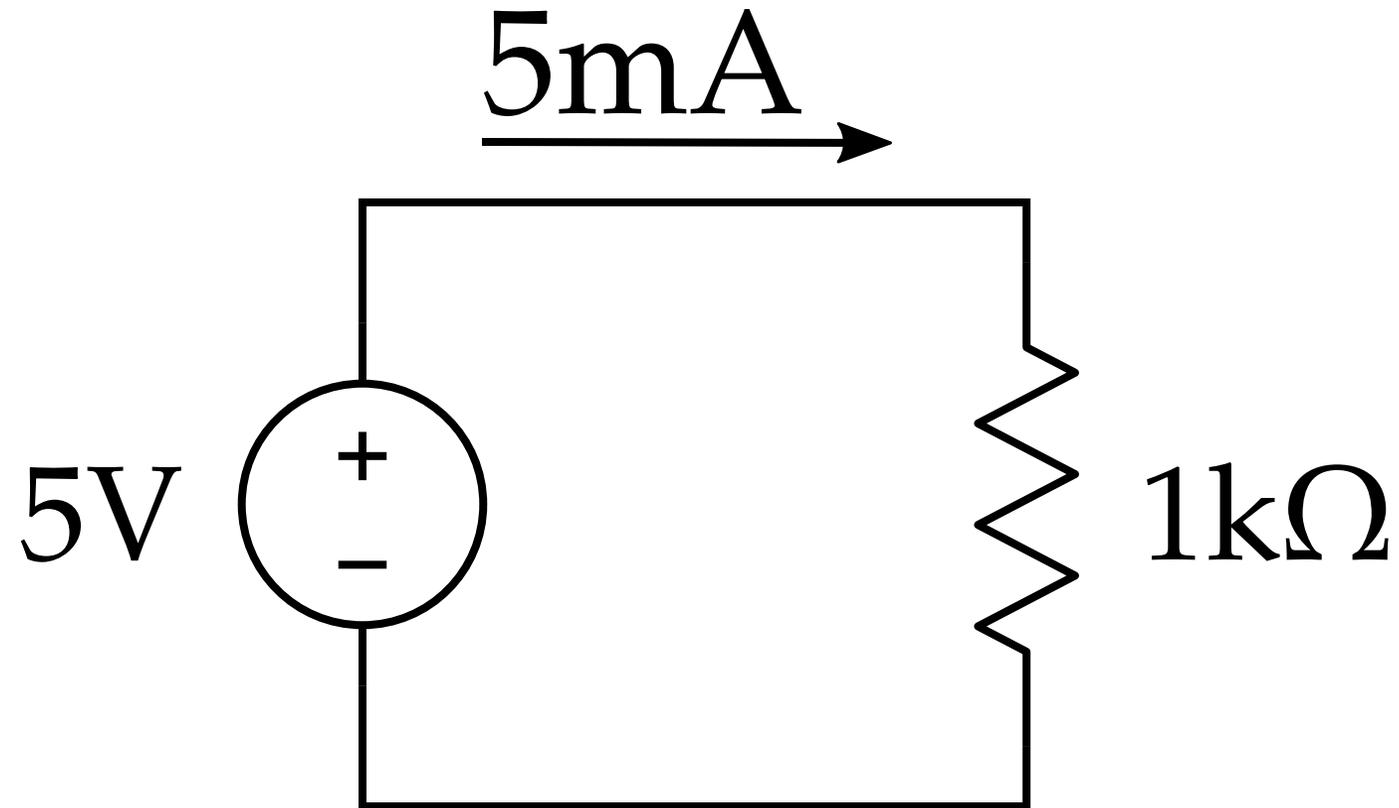How much power does the resistor dissipate?



A more exciting example


Presto Hot Dogger

youtube.com/watch?v=n2ZZbuOeNmww



What happens if you run the Hot Dogger at 240V instead of 120V?

Compare the currents

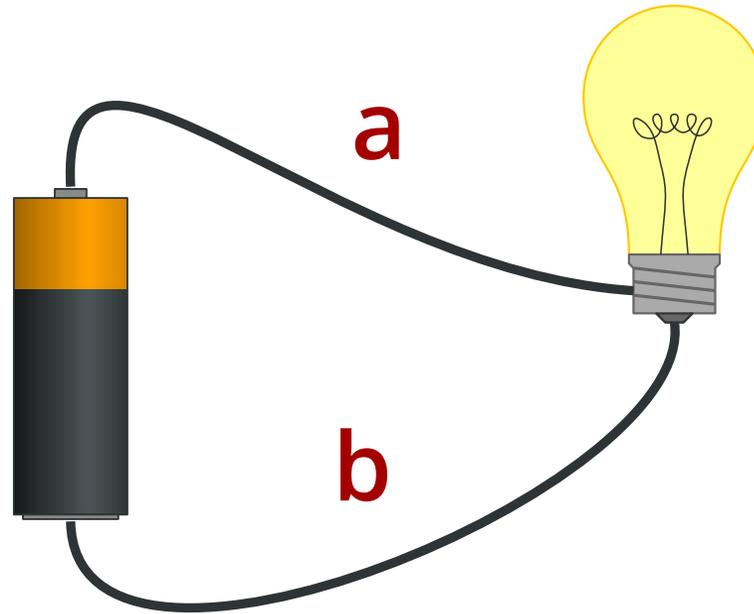

- 1)** The currents are always equal
- 2)** (a) is larger for a split second while electricity flows into the bulb, then the currents are equal
- 3)** (b) is less than (a) because some current is turned into light + heat
- 4)** (a) is less than (b) because electrons flow the opposite way to current

Wrapping up

PollEverywhere: what is one question you have after today's class?