

Name: _____

ES 4 Exam 2 practice problems


Fall 2024

Part 1: Sequential building blocks and VHDL

 - (a) For each of the VHDL code snippets below, draw the circuit that will be created. Each snippet is an architecture for the following entity:

```
entity widget is  
  port (  
    clk : in std_logic;  
    a : in std_logic;  
    b : in std_logic;  
    result : out std_logic);  
end;
```

The schematic elements for latches and D flop-flops are shown below for reference.



- (a) **architecture** first **of** widget **is**
begin
 process(clk)
 if rising_edge(clk) **then**
 result <= a **and** b;
 end if;
 end process;
end;

(b) **architecture** second **of** widget **is**
begin
 process(clk, a, b)
 result <= a **and** b;
 end process;
end;


(c) **architecture** third **of** widget **is**
begin
 process(clk, a, b)
 if(clk = '1') **then**
 result <= a **and** b;
 end if;
 end process;
end;

(d) **architecture** fourth **of** widget **is**
 signal a_tmp : std_logic;
begin
 process(clk)
 if rising_edge(clk) **then**
 a_tmp <= a;
 result <= a_tmp **and** b;
 end if;
 end process;
end;

(e) **architecture** fifth **of** widget **is**
 signal a_tmp : std_logic;
begin
 process(clk)
 if rising_edge(clk) **then**
 result <= a_tmp **and** b;
 end if;
 end process;
 a_tmp <= a;
end;

 Part 2: Writing VHDL


Write VHDL code to create the circuit below. The entity has been started for you.



```
entity countdown is
  port (
    clk : in std_logic;
    select_n : in std_logic;
    result : out unsigned(3 downto 0));
end;

architecture synth of countdown is
begin
```

 Write VHDL code to create the circuit below. The entity has been started for you.



```
entity updown is
  port (
    clk : in std_logic;
    up : in std_logic;
    c : out std_logic;
  end;


  architecture synth of updown is
  begin
```

Part 3: Timing

The iCE40UP5K FPGA has the following timing characteristics¹:

Flip-flop clk-to-Q t_{pd}	1.0 ns
Flip-flop setup time	0.2 ns
Flip-flop hold time	0 ns
LUT input-to-output (A/B/C/D to Z) t_{pd}	0.5 ns

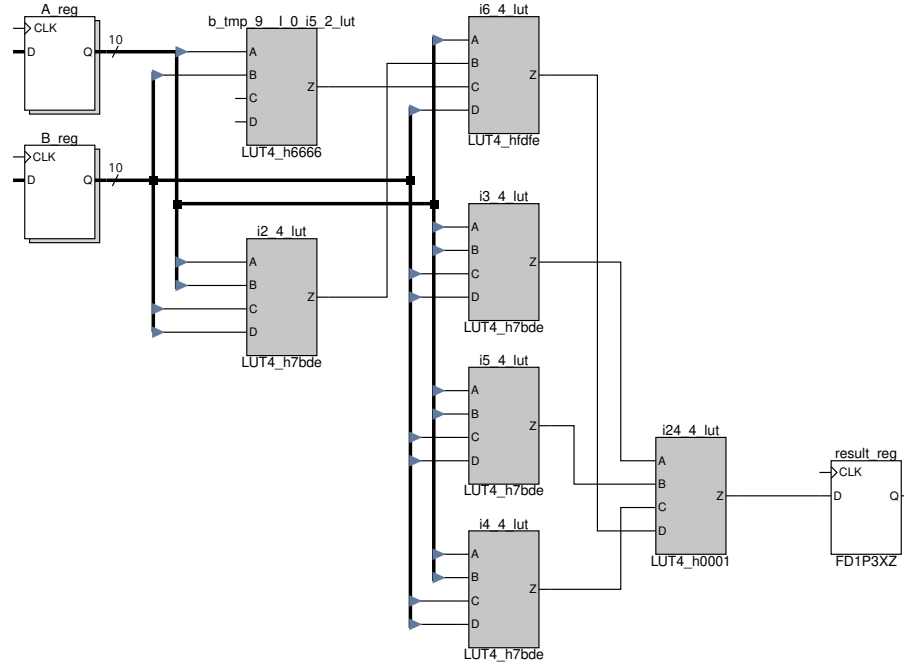The circuit below is an actual FPGA implementation which checks whether two 10-bit signals (stored in A_reg and B_reg) are equal. The bold lines are the 10-bit signals, with individual bits going into the LUTs.



What is the maximum frequency this circuit could be clocked at?

¹These numbers are taken from the Radiant P&R report and rounded for simplicity.

Part 4: Memory

A memory has 8-bit words and a 10-bit address bus. Assuming that all of the possible addresses are valid, how many bits does it store?

Sketch a block diagram for this memory, assuming that it is a single-ported RAM. That is, it can be both read and written, but it's not possible to read and write to different addresses at the same time.