

Warmup

What is $0101\ 0001 + 0000\ 1101$?

Respond at **pollev.com/stevenbell699**

ES 4: Boolean equations and logic gates

Steven Bell

23 January 2019

By the end of class today, you should be able to:

- Write truth tables for AND, OR, XOR, NOT, NAND, NOR, XNOR
- Write a boolean equation from an English description and vice-versa
- Draw a logic diagram from a boolean equation and vice-versa
- Write a truth table from a boolean equation and vice-versa

Key representations


Boolean equation

$$\overline{AB} + C$$

Truth table

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1

Logic diagram

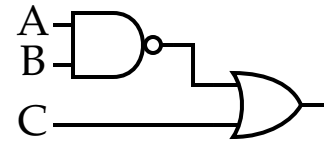

Key representations

English
description

Not both apples and
bananas...

Code

```
!(A&&B) || C
```


Boolean equation

$$\overline{AB} + C$$


Truth table

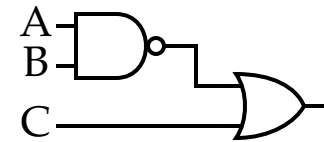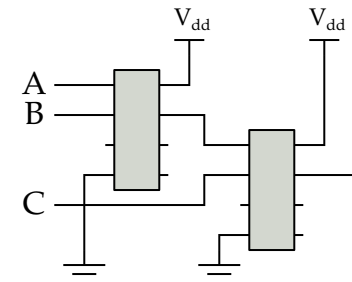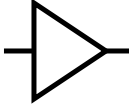
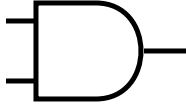
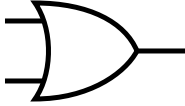
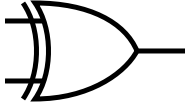
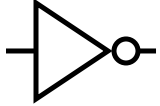

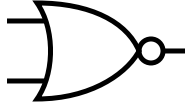
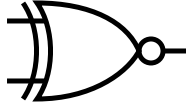
A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1


Logic diagram



Circuit diagram



Name	Buffer	AND	OR	XOR	Inverter	NAND	NOR	XNOR																																																																																																						
Logic symbol																																																																																																														
Logic equation	A	AB	$A+B$	$A\oplus B$	\bar{A}	\overline{AB}	$\overline{A+B}$	$\overline{A\oplus B}$																																																																																																						
Truth table	<table border="1" data-bbox="529 578 616 721"> <thead> <tr><th>A</th><th>Y</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td></tr> </tbody> </table>	A	Y	0	0	1	1	<table border="1" data-bbox="744 578 881 815"> <thead> <tr><th>A</th><th>B</th><th>Y</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	A	B	Y	0	0	0	0	1	0	1	0	0	1	1	1	<table border="1" data-bbox="983 578 1121 815"> <thead> <tr><th>A</th><th>B</th><th>Y</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	A	B	Y	0	0	0	0	1	1	1	0	1	1	1	1	<table border="1" data-bbox="1223 578 1360 815"> <thead> <tr><th>A</th><th>B</th><th>Y</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	Y	0	0	0	0	1	1	1	0	1	1	1	0	<table border="1" data-bbox="1488 578 1574 721"> <thead> <tr><th>A</th><th>Y</th></tr> </thead> <tbody> <tr><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td></tr> </tbody> </table>	A	Y	0	1	1	0	<table border="1" data-bbox="1702 578 1839 815"> <thead> <tr><th>A</th><th>B</th><th>Y</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	Y	0	0	1	0	1	1	1	0	1	1	1	0	<table border="1" data-bbox="1941 578 2079 815"> <thead> <tr><th>A</th><th>B</th><th>Y</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	Y	0	0	1	0	1	0	1	0	0	1	1	0	<table border="1" data-bbox="2181 578 2318 815"> <thead> <tr><th>A</th><th>B</th><th>Y</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	A	B	Y	0	0	1	0	1	0	1	0	0	1	1	1
A	Y																																																																																																													
0	0																																																																																																													
1	1																																																																																																													
A	B	Y																																																																																																												
0	0	0																																																																																																												
0	1	0																																																																																																												
1	0	0																																																																																																												
1	1	1																																																																																																												
A	B	Y																																																																																																												
0	0	0																																																																																																												
0	1	1																																																																																																												
1	0	1																																																																																																												
1	1	1																																																																																																												
A	B	Y																																																																																																												
0	0	0																																																																																																												
0	1	1																																																																																																												
1	0	1																																																																																																												
1	1	0																																																																																																												
A	Y																																																																																																													
0	1																																																																																																													
1	0																																																																																																													
A	B	Y																																																																																																												
0	0	1																																																																																																												
0	1	1																																																																																																												
1	0	1																																																																																																												
1	1	0																																																																																																												
A	B	Y																																																																																																												
0	0	1																																																																																																												
0	1	0																																																																																																												
1	0	0																																																																																																												
1	1	0																																																																																																												
A	B	Y																																																																																																												
0	0	1																																																																																																												
0	1	0																																																																																																												
1	0	0																																																																																																												
1	1	1																																																																																																												
C++ equivalent	A	$A\&\&B$	$A B$	$A!=B$	$!A$	$!(A\&\&B)$	$!(A B)$	$A==B$																																																																																																						
74-series IC	7407	7408	7432	7486	7404	7400	7402	various																																																																																																						

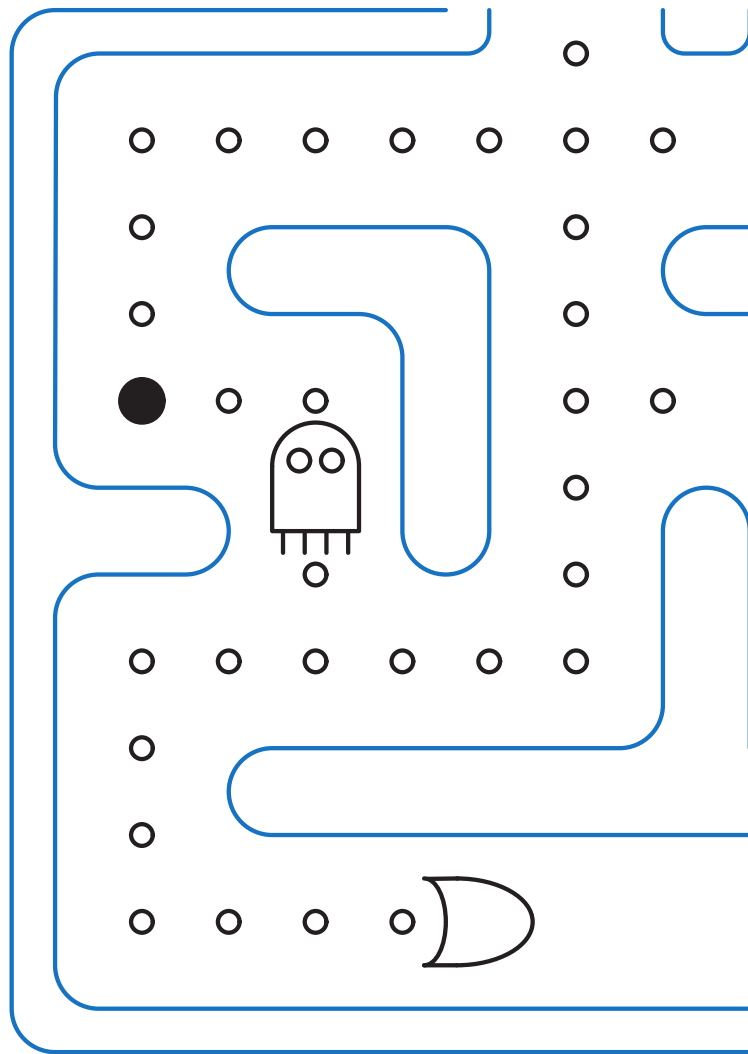

Pacman is like an OR gate...?



STAR TREK

Y

STORY TREK

A

B

Bigger equations

We'll use a **bar** to indicate inversion: $\overline{A+B}$

You might also see "¬" for inversion: $\neg(A+B)$

AND takes precedence over OR:

$$AB + C = (AB) + C$$

(Think multiplication over addition)

Combining gates

Elements are objects:

Nodes are the interconnections:

Wires are connected if there's a dot:

What is combinational?

A circuit is combinational if:

1. It is a discrete logic gate, or
2. It is composed of combinational elements such that:
 - There are no cycles, and
 - Every node (wire) is only driven by one gate

Who cares, anyway?


In a combinational circuit,
outputs are a function of only the current inputs

Feedback loops can break this!


Driving one wire with multiple gates breaks the digital abstraction!

Which of the circuits below are combinational?


(1)

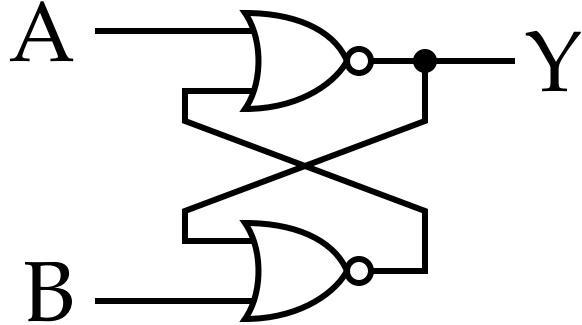


(2)

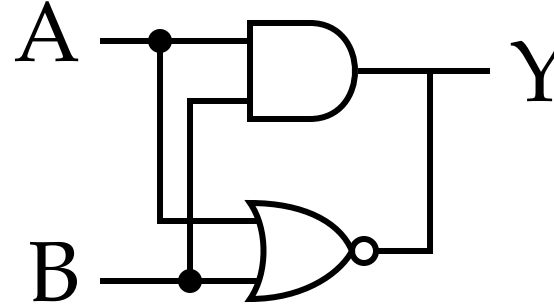

(3)

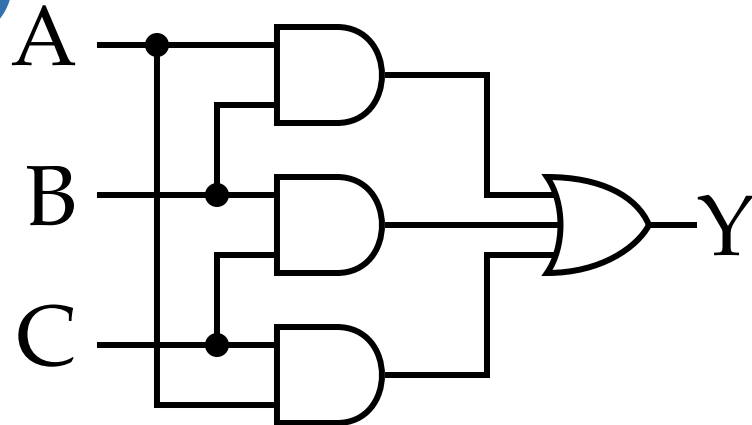

(4)

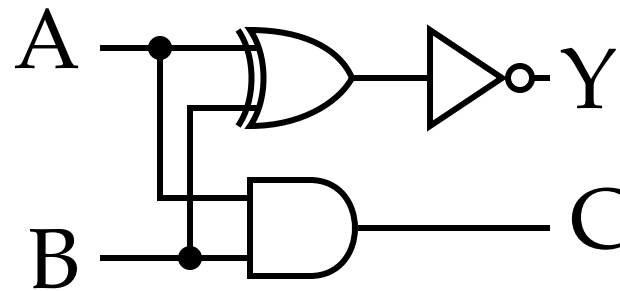


Respond at pollev.com/stevenbell699


Translating representations

Boolean equation

$$\overline{AB} + C$$

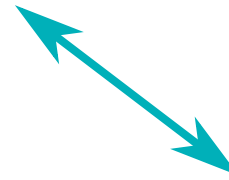

Logic diagram

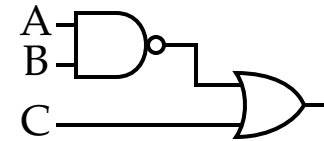

Truth table

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1

Boolean equation \leftrightarrow logic diagram

Replace operations with gates, following precedence

Replace gates with operations, nesting to create precedence

Translating representations

Boolean equation


$$\overline{AB} + C$$

Evaluate


Truth table

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1


Logic diagram

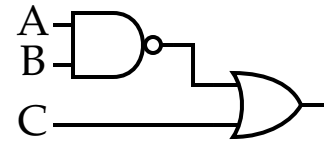

Translating representations

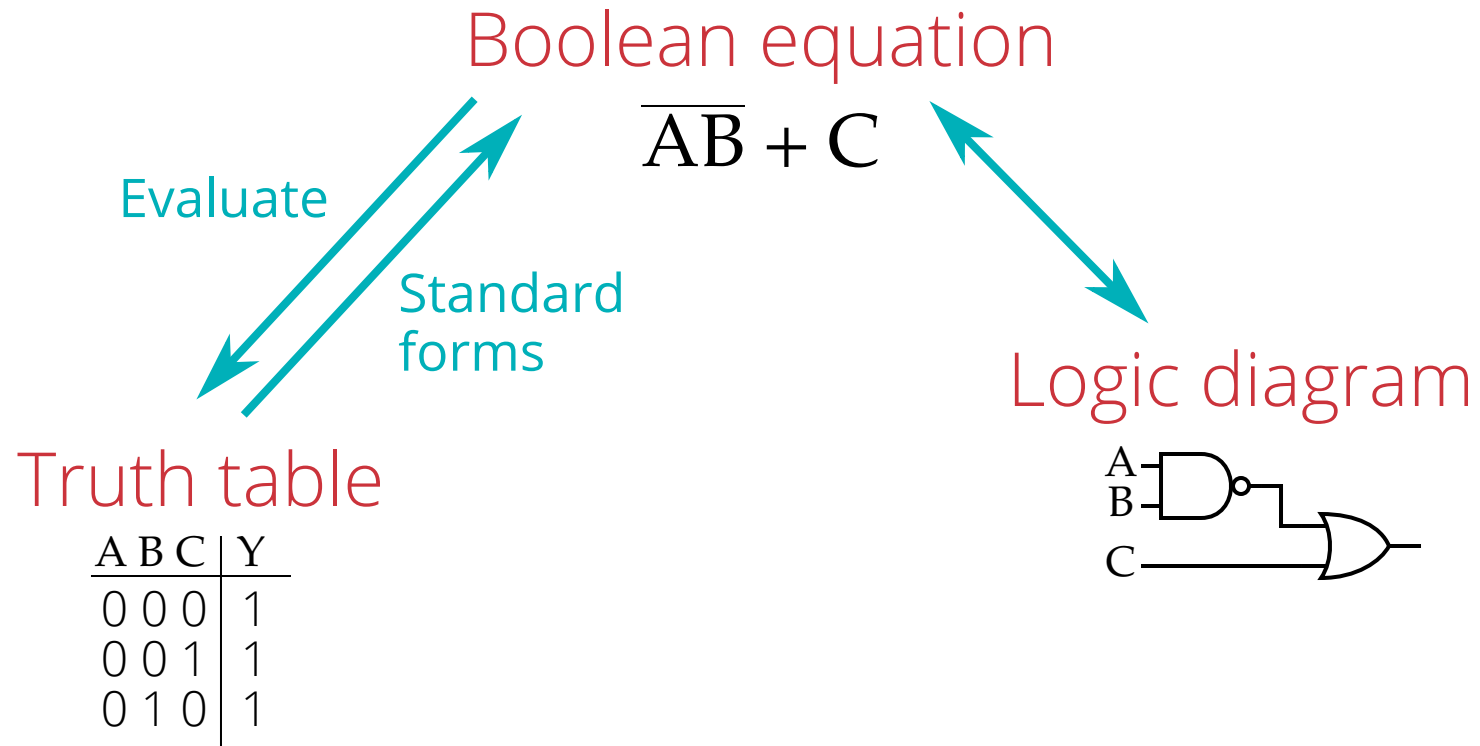

Translating representations

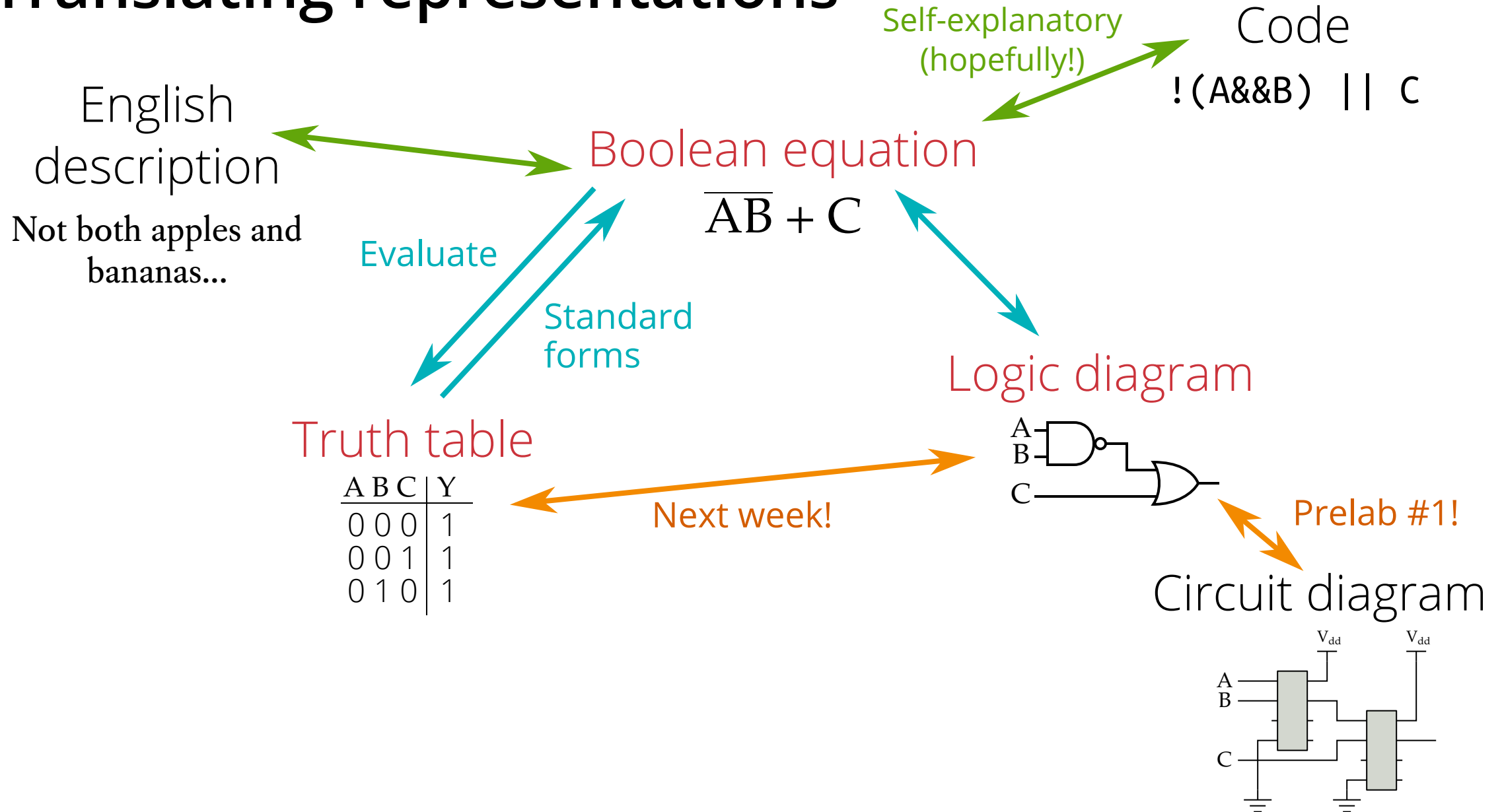

A useful circuit

We have two 2-bit numbers. Design a circuit to calculate $A > B$.

Lab process

- 1) Submit your prelab on Gradescope, 24 hours in advance
- 2) Show up and work on your lab during your assigned lab time
- 3) Turn in your lab report two weeks from today (2/6)

For Monday

1. Read the book (2.3-2.7) and complete the pre-class quiz

www.ece.tufts.edu/es/4/

Quiz is due at **9AM** the day of class, so I can review it

```
cp /es/4/public_html/quizzes/quiz_02.txt ./
```

```
provide es4 q2 quiz_02.txt
```

Boolean or boolean?



George Boole
(1815-1864)

(Photo from Wikimedia)

Why is NAND a big deal?



For the purposes of this course,

MOS transistors are electrically-controlled **switches**.


They have one terminal that controls the "switch", called the **gate**.

When the transistor is on, current can flow between the other terminals, called the **source** and **drain**.

They come in two types:

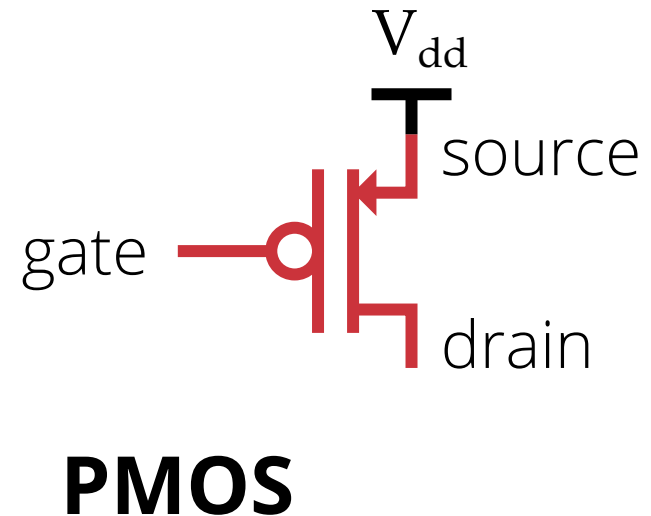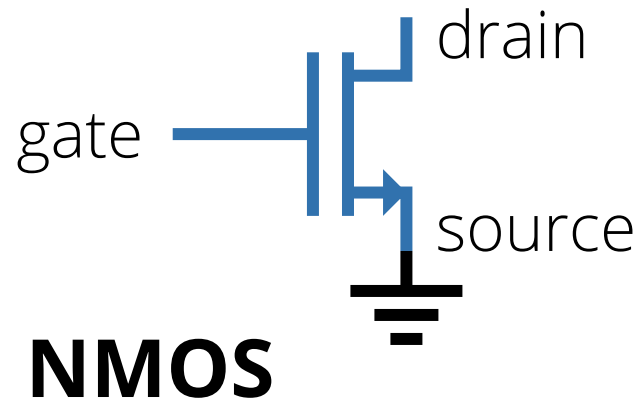

A simple gate

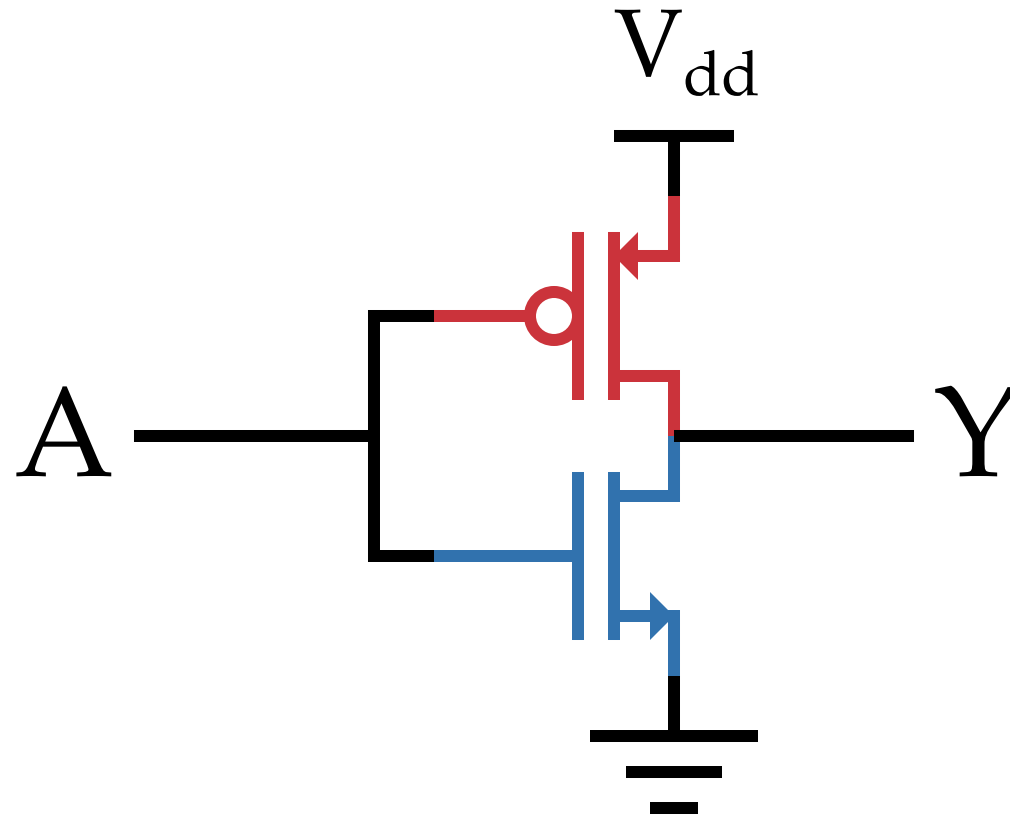

PMOS: "closed" when gate is **low**.

NMOS: "closed" when gate is **high**.

A more complex gate

