

# Warmup

$$\begin{array}{r} \overset{\cdot}{1} \overset{\cdot}{1} \overset{\cdot}{1} \overset{\cdot}{1} \\ + \quad 1 \quad 1 \quad 1 \\ \hline 1 \quad 1 \quad 1 \quad 0 \end{array} \quad \begin{array}{r} 7 \\ 7 \\ \hline 14 \end{array}$$

# ES 4: Boolean equations and logic gates

Steven Bell

5 September 2024

# Nervous about

- Workload / time needed for solid understanding  
"I've never taken this many credits before..."
- Background / content being new  
"This course was required for my major, but I know very little about it..."
- Building circuits  
"I've never worked with circuit hardware before..."

# From the reading check

- What good are sum-of-products and product-of-sums?
- minterms, pls explain.
- How do I tell if something is combinational?
- How do I go about memorizing the difference between NOT, AND, OR, XOR, NAND, NOR, XNOR?

# By the end of class today, you should be able to:

- Write truth tables for AND, OR, XOR, NOT, NAND, NOR, XNOR
- Write a boolean equation from an English description and vice-versa
- Draw a logic diagram from a boolean equation and vice-versa
- Write a truth table from a boolean equation and vice-versa

# Key representations


Boolean equation

$$\overline{AB} + C$$

Truth table

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1

Logic diagram

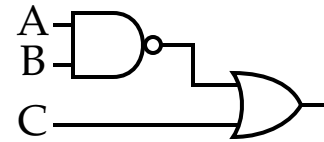

# Key representations

English  
description

Not both apples and  
bananas...

Code  
`!(A&&B) || C`


Boolean equation

$$\overline{AB} + C$$


Truth table

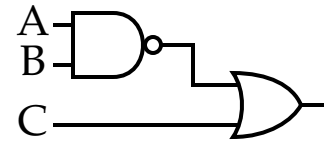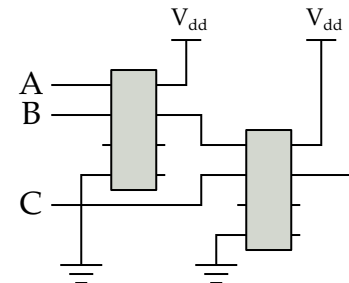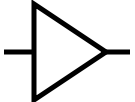

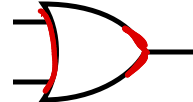
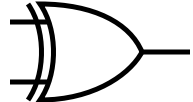
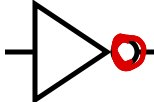

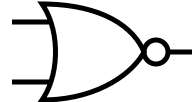
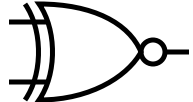
A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1


Logic diagram



Circuit diagram



Name	Buffer	AND	OR	XOR	<i>NOT</i> Inverter	<i>Inverted</i> NAND	NOR	XNOR																																																																																																						
Logic symbol																																																																																																														
Logic equation	$A$	$AB$	$A+B$	$A \oplus B$ <i>⊕ plus</i>	$\bar{A}$	$\overline{AB}$	$\overline{A+B}$	$\overline{A \oplus B}$																																																																																																						
Truth table	<table border="1" data-bbox="522 578 624 721"> <thead> <tr><th>A</th><th>Y</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td></tr> </tbody> </table>	A	Y	0	0	1	1	<table border="1" data-bbox="738 578 879 813"> <thead> <tr><th>A</th><th>B</th><th>Y</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	A	B	Y	0	0	0	0	1	0	1	0	0	1	1	1	<table border="1" data-bbox="980 578 1121 813"> <thead> <tr><th>A</th><th>B</th><th>Y</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	A	B	Y	0	0	0	0	1	1	1	0	1	1	1	1	<table border="1" data-bbox="1210 578 1363 813"> <thead> <tr><th>A</th><th>B</th><th>Y</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	Y	0	0	0	0	1	1	1	0	1	1	1	0	<table border="1" data-bbox="1477 578 1579 721"> <thead> <tr><th>A</th><th>Y</th></tr> </thead> <tbody> <tr><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td></tr> </tbody> </table>	A	Y	0	1	1	0	<table border="1" data-bbox="1694 578 1834 813"> <thead> <tr><th>A</th><th>B</th><th>Y</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	Y	0	0	1	0	1	1	1	0	1	1	1	0	<table border="1" data-bbox="1923 578 2076 813"> <thead> <tr><th>A</th><th>B</th><th>Y</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	Y	0	0	1	0	1	0	1	0	0	1	1	0	<table border="1" data-bbox="2165 578 2318 813"> <thead> <tr><th>A</th><th>B</th><th>Y</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	A	B	Y	0	0	1	0	1	0	1	0	0	1	1	1
A	Y																																																																																																													
0	0																																																																																																													
1	1																																																																																																													
A	B	Y																																																																																																												
0	0	0																																																																																																												
0	1	0																																																																																																												
1	0	0																																																																																																												
1	1	1																																																																																																												
A	B	Y																																																																																																												
0	0	0																																																																																																												
0	1	1																																																																																																												
1	0	1																																																																																																												
1	1	1																																																																																																												
A	B	Y																																																																																																												
0	0	0																																																																																																												
0	1	1																																																																																																												
1	0	1																																																																																																												
1	1	0																																																																																																												
A	Y																																																																																																													
0	1																																																																																																													
1	0																																																																																																													
A	B	Y																																																																																																												
0	0	1																																																																																																												
0	1	1																																																																																																												
1	0	1																																																																																																												
1	1	0																																																																																																												
A	B	Y																																																																																																												
0	0	1																																																																																																												
0	1	0																																																																																																												
1	0	0																																																																																																												
1	1	0																																																																																																												
A	B	Y																																																																																																												
0	0	1																																																																																																												
0	1	0																																																																																																												
1	0	0																																																																																																												
1	1	1																																																																																																												
C++ equivalent	$A$	$A \& \& B$	$A \mid \mid B$	$A \neq B$	$!A$	$!(A \& \& B)$	$!(A \mid \mid B)$	$A == B$																																																																																																						
74-series IC	7407	7408	7432	7486	7404	7400	7402	various																																																																																																						

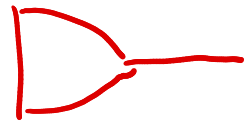





STAR TREK



Y

A

B

# Bigger equations

We'll use a **bar** to indicate inversion:  $\overline{A+B}$

You might also see "¬" for inversion:  $\neg(A+B)$

AND takes precedence over OR:

$$AB + C = (AB) + C$$

(Think multiplication over addition)

$$A(B+C)$$


Set theory uses  $\wedge$  and  $\vee$  for AND and OR respectively.

# Drawing logic diagrams

**Elements** are objects

**Nodes** are the interconnections

$$Y = (AB) + (\overline{B}C)$$

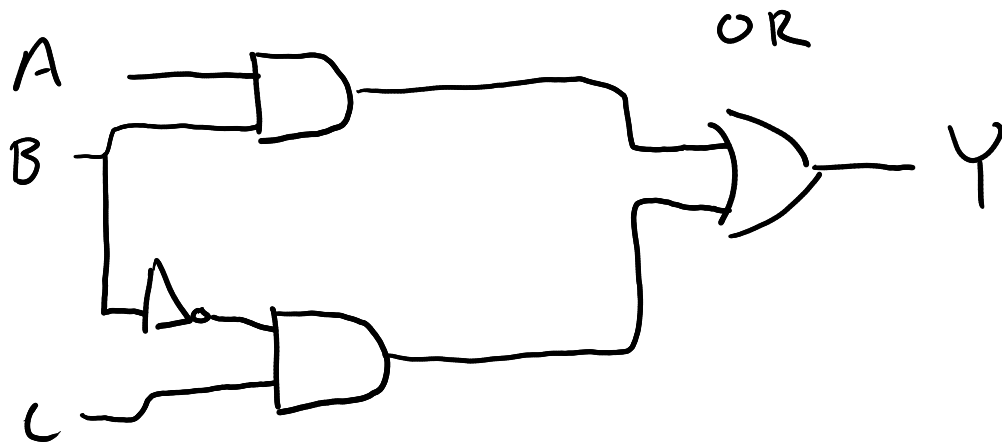


# Drawing logic diagrams

**Elements** are objects

**Nodes** are the interconnections

$$Y = AB + \overline{B}\overline{C}$$

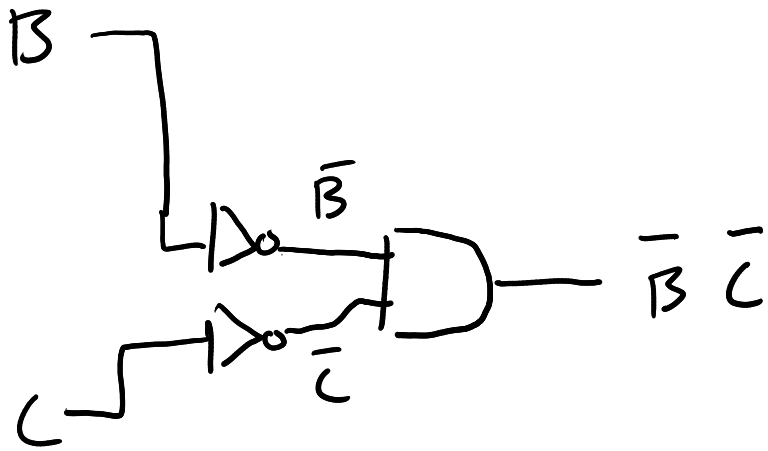


$B$	$C$	$\overline{B}$	$\overline{C}$	$\overline{B}\overline{C}$	$\overline{BC}$
0	0	1	1	1	1
0	1	1	0	0	1
1	0	0	1	0	1
1	1	0	0	0	0


NAND

# Logic diagram connections


Wires are connected if there's a dot:

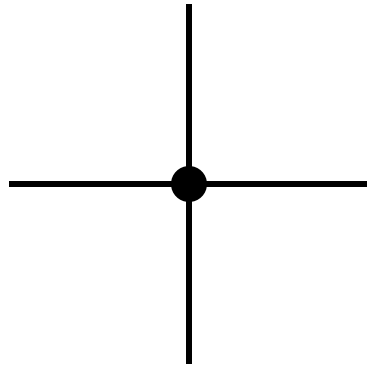


connected

 

not connected

 

connected

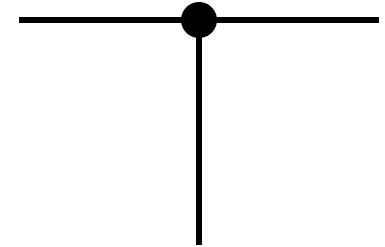

connected  
(dot is only for clarity)


# What is combinational?

A circuit is combinational if:


1. It is a discrete logic gate, or
2. It is composed of combinational elements such that:
  - There are no cycles, and
  - Every node (wire) is only driven by one gate

Which of the circuits below are combinational?


(1)

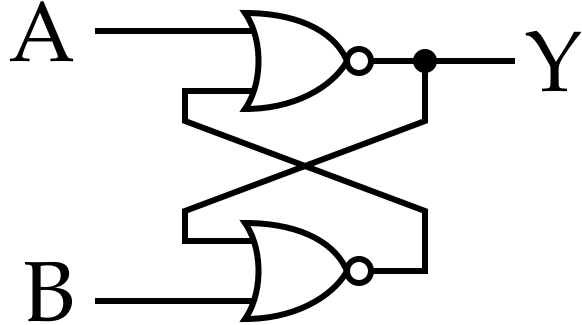


(2)

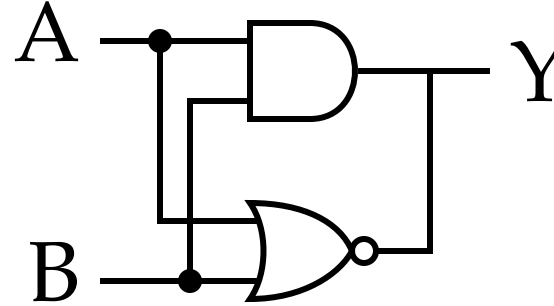

(3)

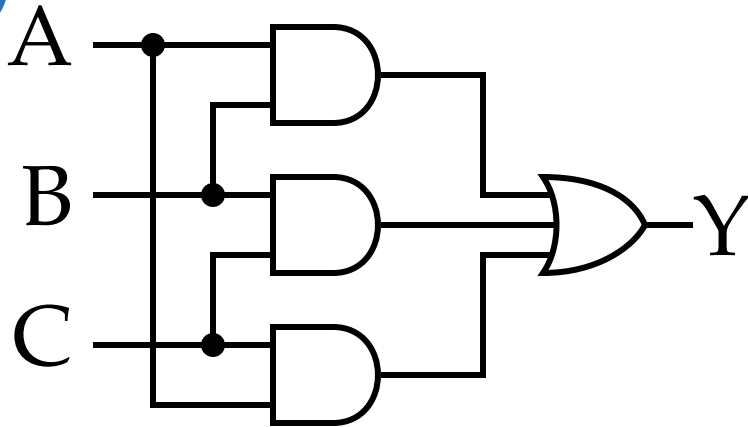

(4)

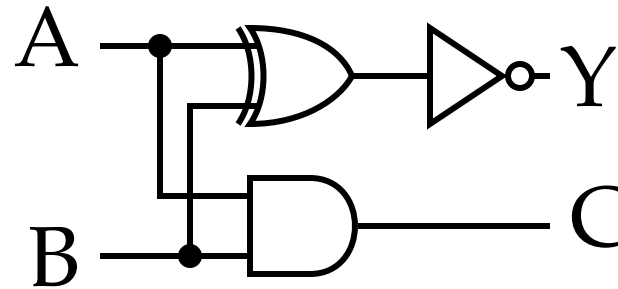

Respond at [pollev.com/stevenbell](https://pollev.com/stevenbell)

# Who cares, anyway?

In a combinational circuit,  
outputs are a function of **only the current inputs**


Feedback loops can break this!

Driving one wire with multiple gates breaks the digital abstraction!


# Translating representations

Boolean equation

$$\overline{AB} + C$$

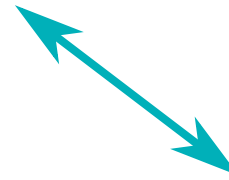

Logic diagram

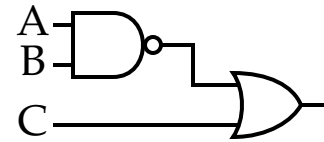

Truth table

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1

# Boolean equation $\leftrightarrow$ logic diagram

Replace operations with gates, following precedence

Replace gates with operations, nesting to create precedence

# Translating representations

Boolean equation


$$\overline{AB} + C$$

Evaluate

Truth table

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1

Logic diagram

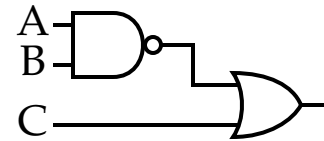


# Boolean equation to truth table

$$Y = AB + \bar{C}$$

A	B	C	AB	Y
0	0	0	0	1
0	0	1	0	0
0	1	0	0	1
0	1	1	0	0
1	0	0	0	1
1	0	1	0	0
1	1	0	1	1
1	1	1	1	1

# Translating representations

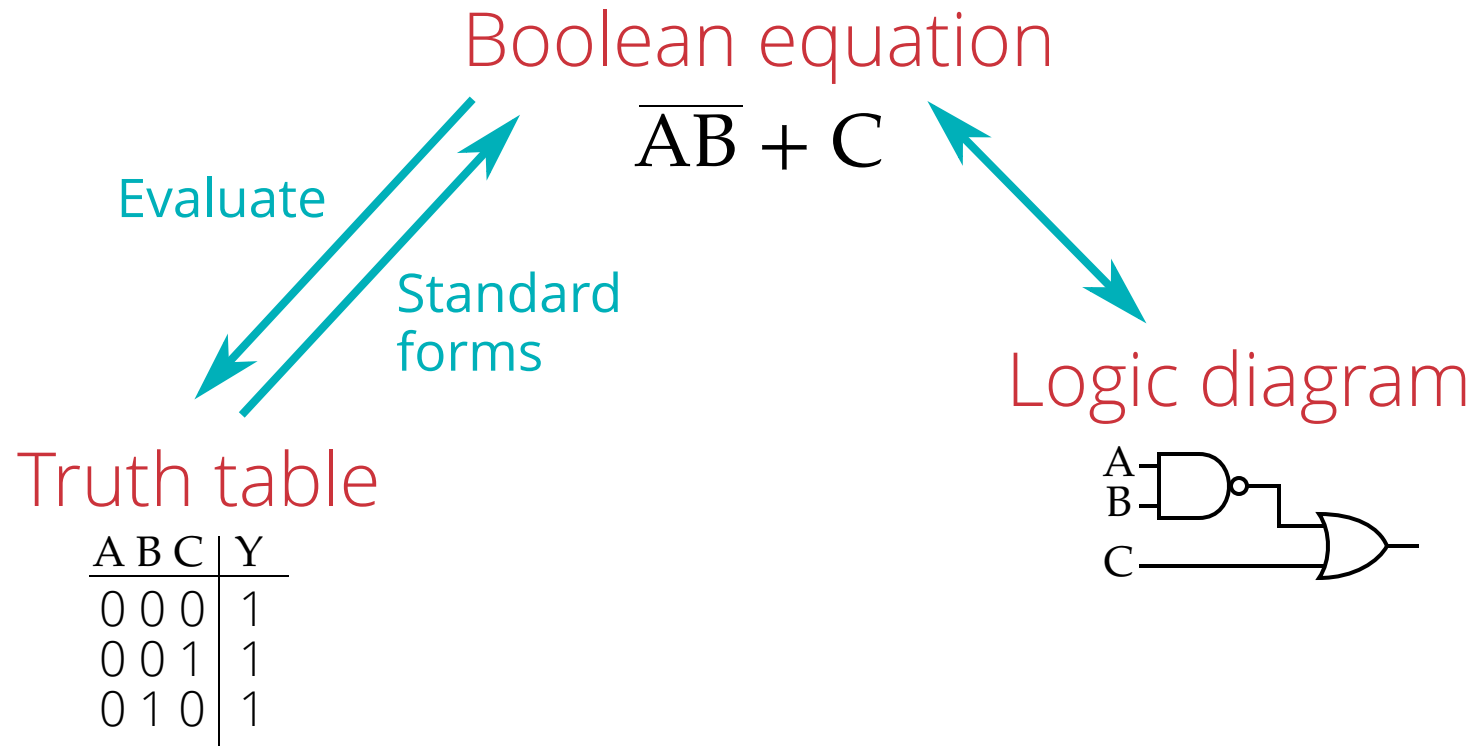

# Truth table to boolean equation



A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

$$\bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C} = Y$$

# Truth table to boolean equation

$$Y = (\bar{A} + \bar{B} + \bar{C}) (A + \bar{B} + C) (\bar{A} + B + C)$$

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

1  
1  
1  
1  
1  
1  
1  
0

# Truth table to boolean equation

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

$$(A + \bar{B} + C)$$


1  
1  
0

$$(\bar{A} + \bar{B} + C) = Y$$

1  
1  
1  
1  
1  
1  
0  
1

1  
1  
0  
1  
1  
1  
0  
1

# Translating representations

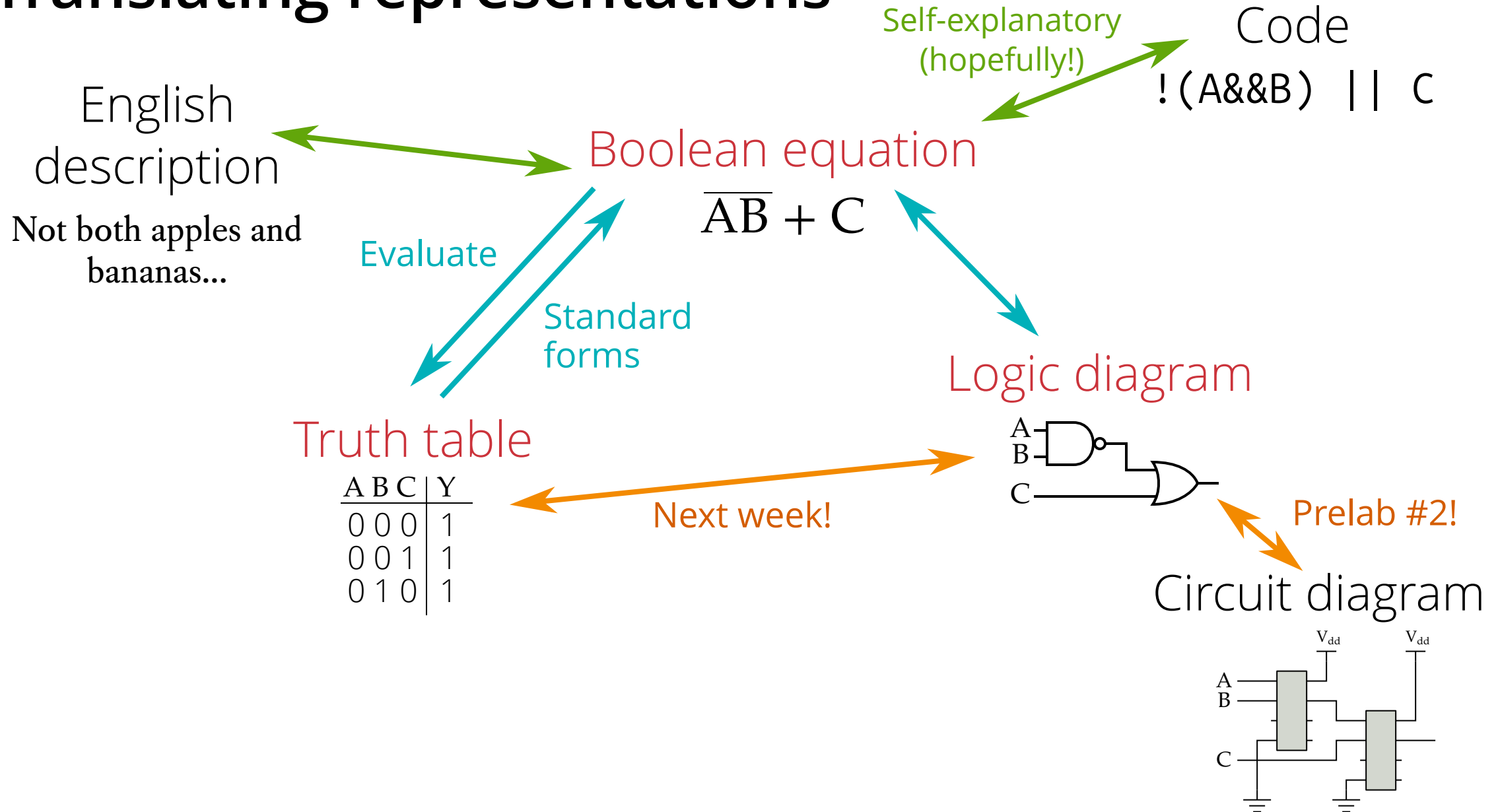

# For next week

1. Read the book (2.3-2.7) and complete the pre-class reading check  
Due at **11 AM** the day of class, so I can review it
2. Welcome survey posted as soon as I finalize lab times
3. Plan to come to lab next week!

# **Bonus material**

Backup slides, extra information, or just stuff  
I had to cut out of the lecture for the sake of time.

# A useful circuit

We have two 2-bit numbers. Design a circuit to calculate  $A > B$ .

# Boolean or boolean?



George Boole  
(1815-1864)

(Photo from Wikimedia)

**Why is NAND a big deal?**



For the purposes of this course,

**MOS transistors** are electrically-controlled **switches**.


They have one terminal that controls the "switch", called the **gate**.

When the transistor is on, current can flow between the other terminals, called the **source** and **drain**.

They come in two types:

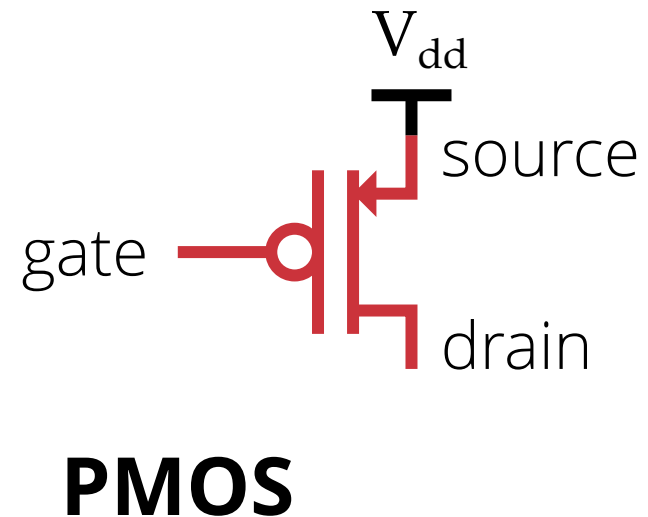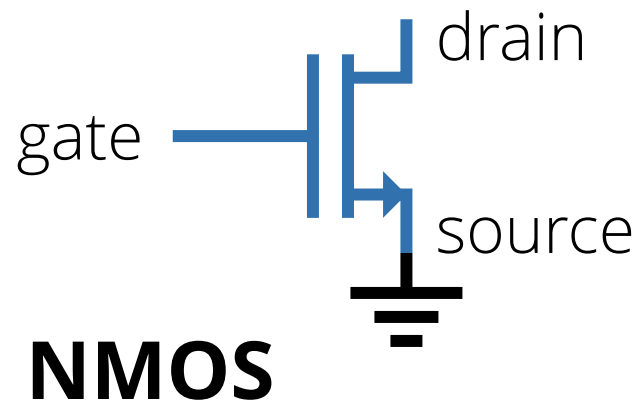

# A simple gate

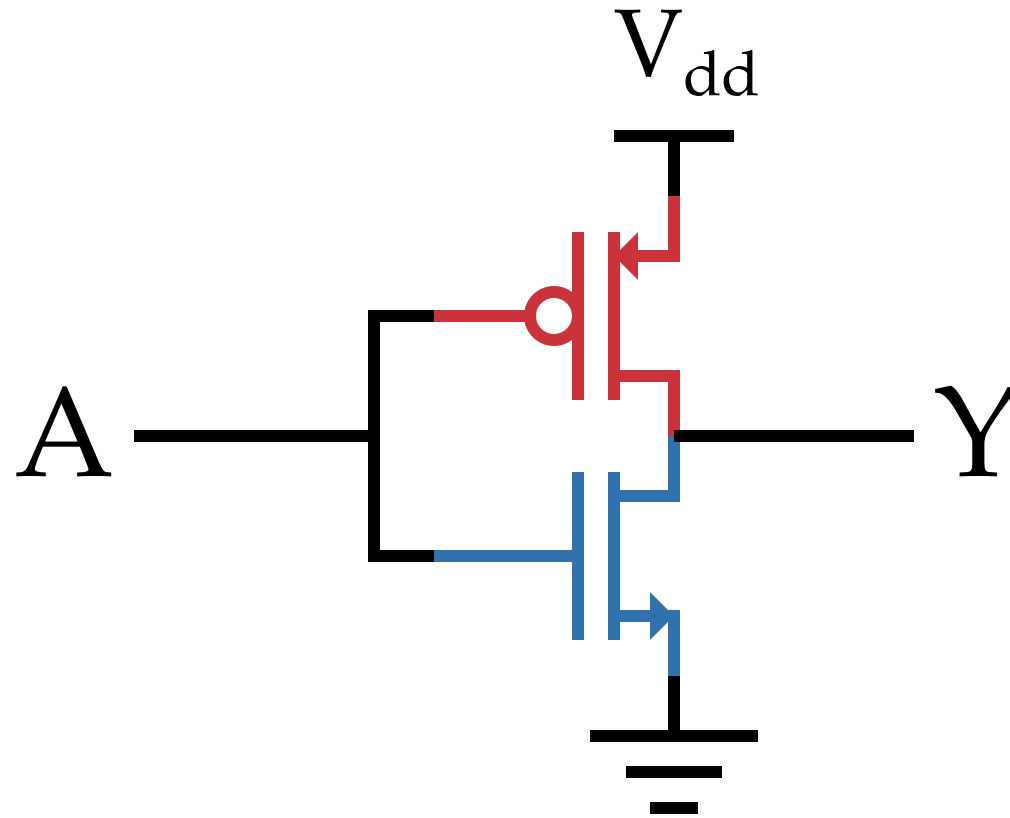

**PMOS:** "closed" when gate is **low**.

**NMOS:** "closed" when gate is **high**.

# A more complex gate

