

Warmup



Use a k-map to find a minimal implementation of this truth table:

A	B	C	D		Y	A	B	C	D		Y
0	0	0	0		0	1	0	0	0		0
0	0	0	1		0	1	0	0	1		1
0	0	1	0		1	1	0	1	0		0
0	0	1	1		1	1	0	1	1		1
0	1	0	0		0	1	1	0	0		0
0	1	0	1		0	1	1	0	1		1
0	1	1	0		1	1	1	1	0		0
0	1	1	1		1	1	1	1	1		1

Respond at pollev.com/stevenbell

Preview of lab 4

4-bit binary
number

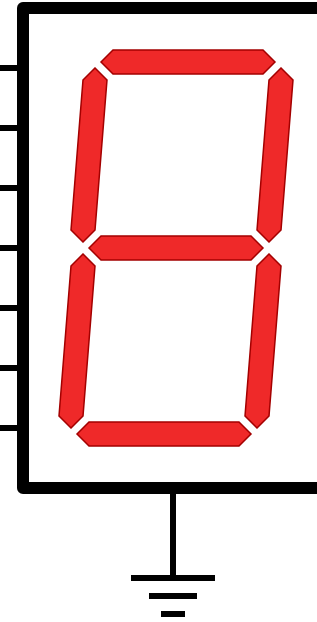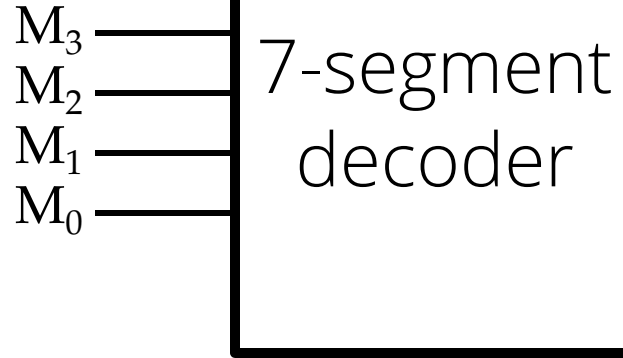

1 0 0 1
~~0 1 0 1~~


= 9

M_3 M_2 M_1 M_0


$8M_3 + 4M_2 + 2M_1 + M_0$

Most
significant
bit (MSB)


Least
significant
bit (LSB)

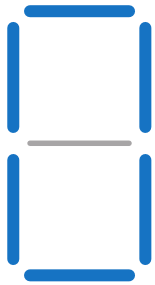

0

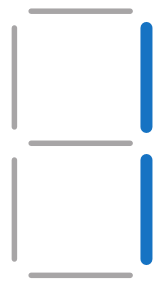


1

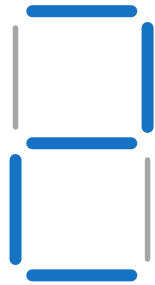

2



3

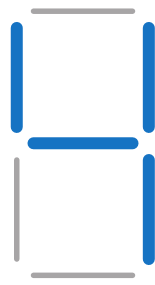

4



5



6





7



8



9

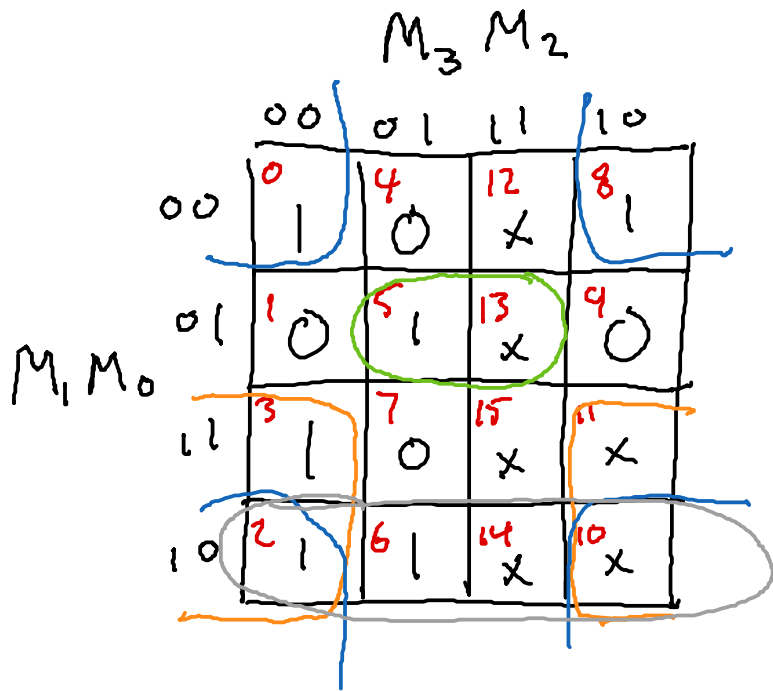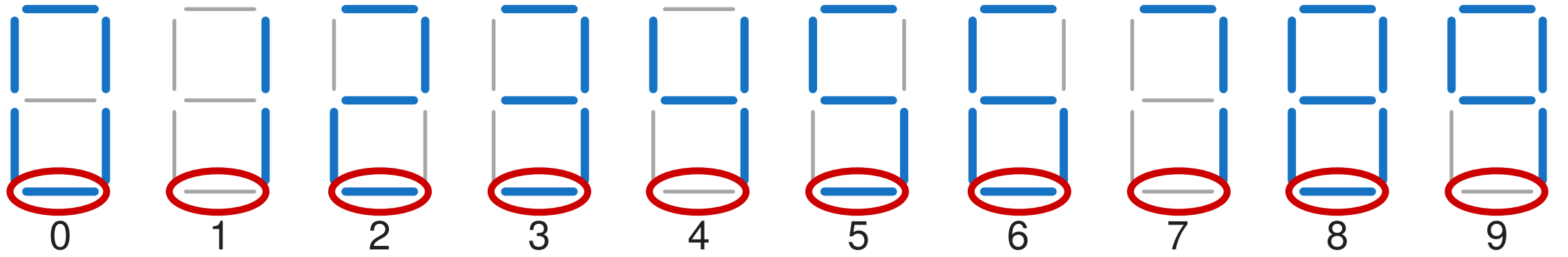

$$M_2 \overline{M_1} M_0$$

$$\overline{M_2} \overline{M_0}$$

ES 4: Multiplexers and FPGAs

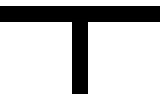

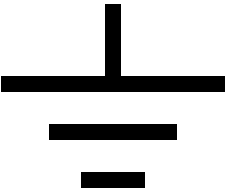
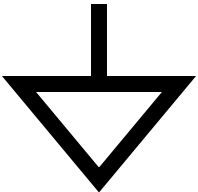
Steven Bell

22 September 2021

By the end of class today, you should be able to:


- Explain what a multiplexer is
- Draw a logic diagram using a 2^N -input multiplexer to implement an N-variable or (N+1)-variable boolean equation
- Describe the basic structure of an FPGA

Some schematic terminology

V_{dd} 		VDD	5V	HIGH	1
		Ground	0V	LOW	0

Multiplexers

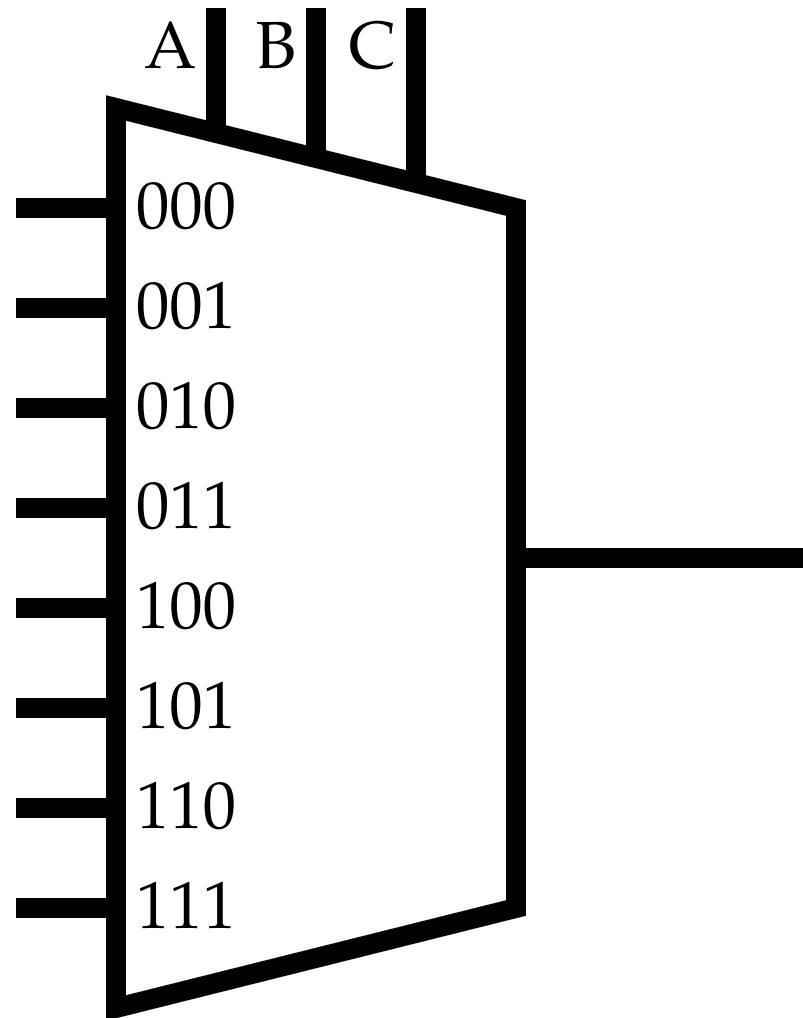Select one of 2^N inputs based on the binary value of N control wires




What good are multiplexers?

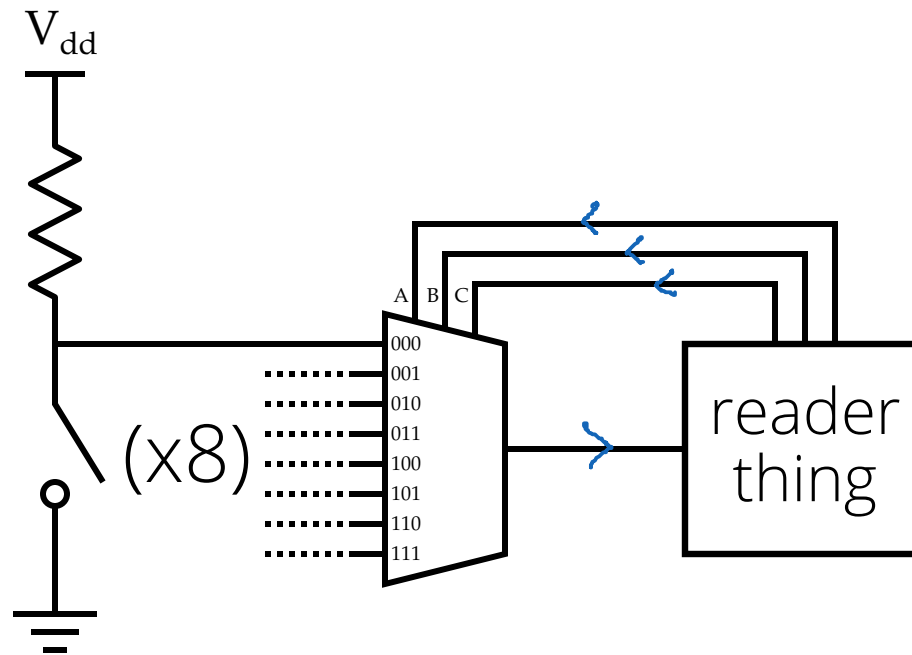1) Allow you to select (or control) one signal out of many

A practical example

Suppose you want to read 8 switches but you only have 4 inputs/outputs.




What good are multiplexers?

1) Allow you to select (or control) one signal out of many

1B) Allow you to make a choice based on a control value

It's like an **if** or **case** statement in software
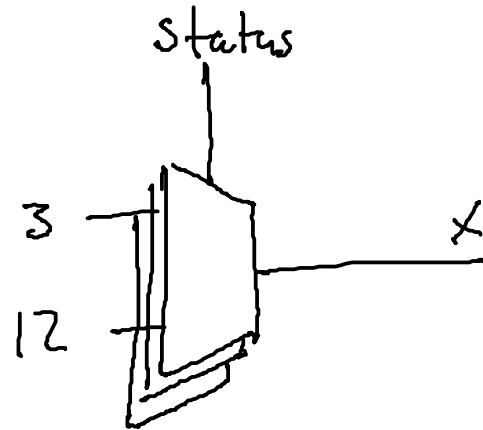
```
if (status == 1) {  
    x = 12;  
} else {  
    x = 3;  
}
```



What good are multiplexers?

1) Allow you to select (or control) one signal out of many


1 B) Allow you to make a choice based on a control value

It's like an **if** or **case** statement in software

2) Make it easy to implement arbitrary logic functions

Implementing XOR

Using a mux as a look-up table (LUT)

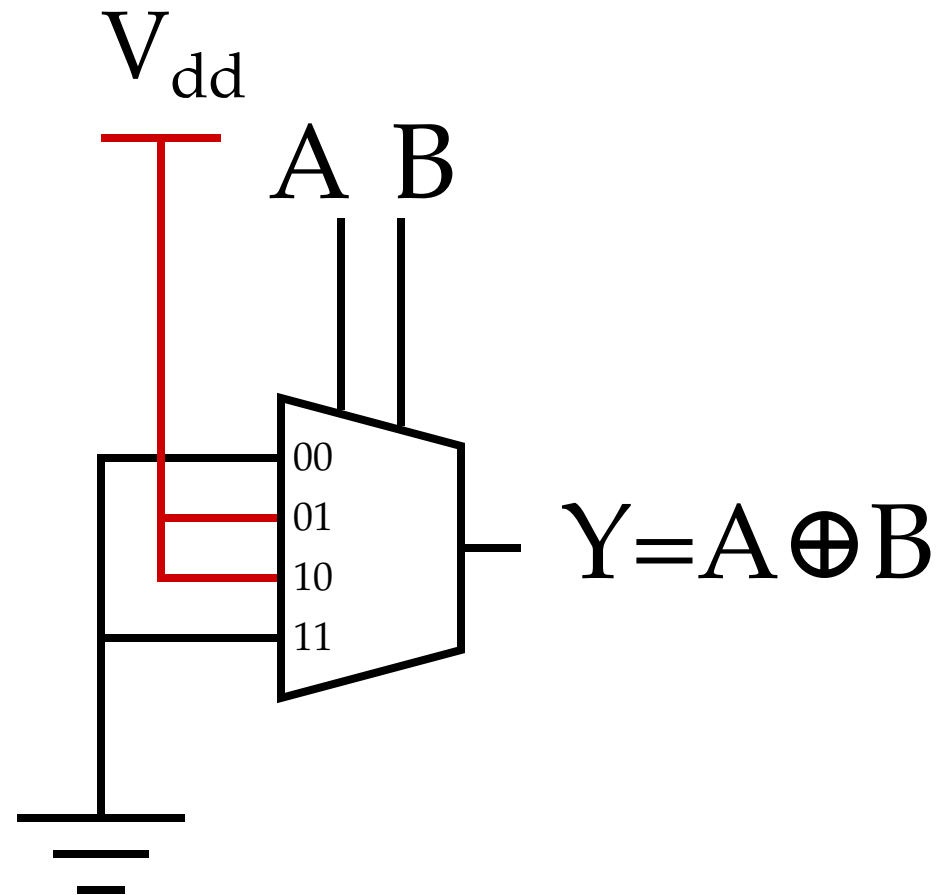



Multiplexer practice 1

Implement this logic equation using

- 1) 8:1 multiplexer
- 2) 4:1 multiplexer

$$Y = \bar{A}B + A\bar{B}\bar{C}$$

A	B	C	$\bar{A}B$	$A\bar{B}\bar{C}$	Y
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	1	0	1
0	1	1	1	0	1
1	0	0	0	1	1
1	0	1	0	0	0
1	1	0	0	0	0
1	1	1	0	0	0

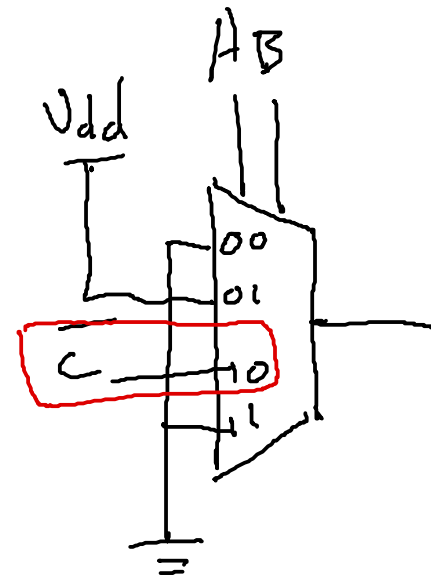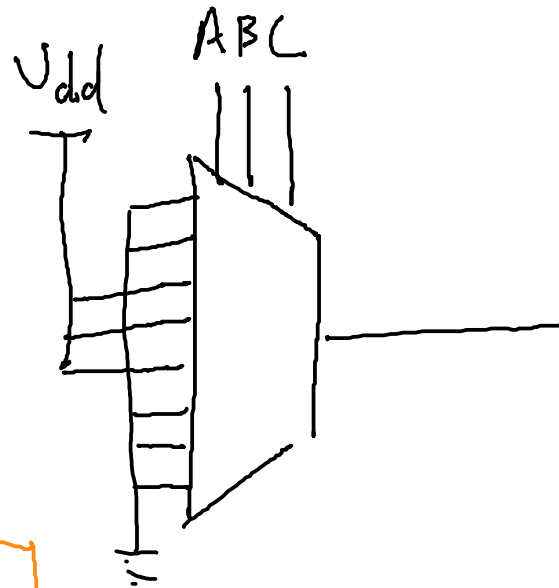

Implement a 2-bit adder with multiplexers (Prelab 3)

How are you feeling about multiplexers?

Respond at pollev.com/stevenbell

Will a time come when it's cheaper to use a microprocessor than to implement something with discrete logic gates?

iCE40UP block diagram

Clock stuff

Fixed-function multipliers

Memory

Logic "fabric"

Fixed-function I/O modules

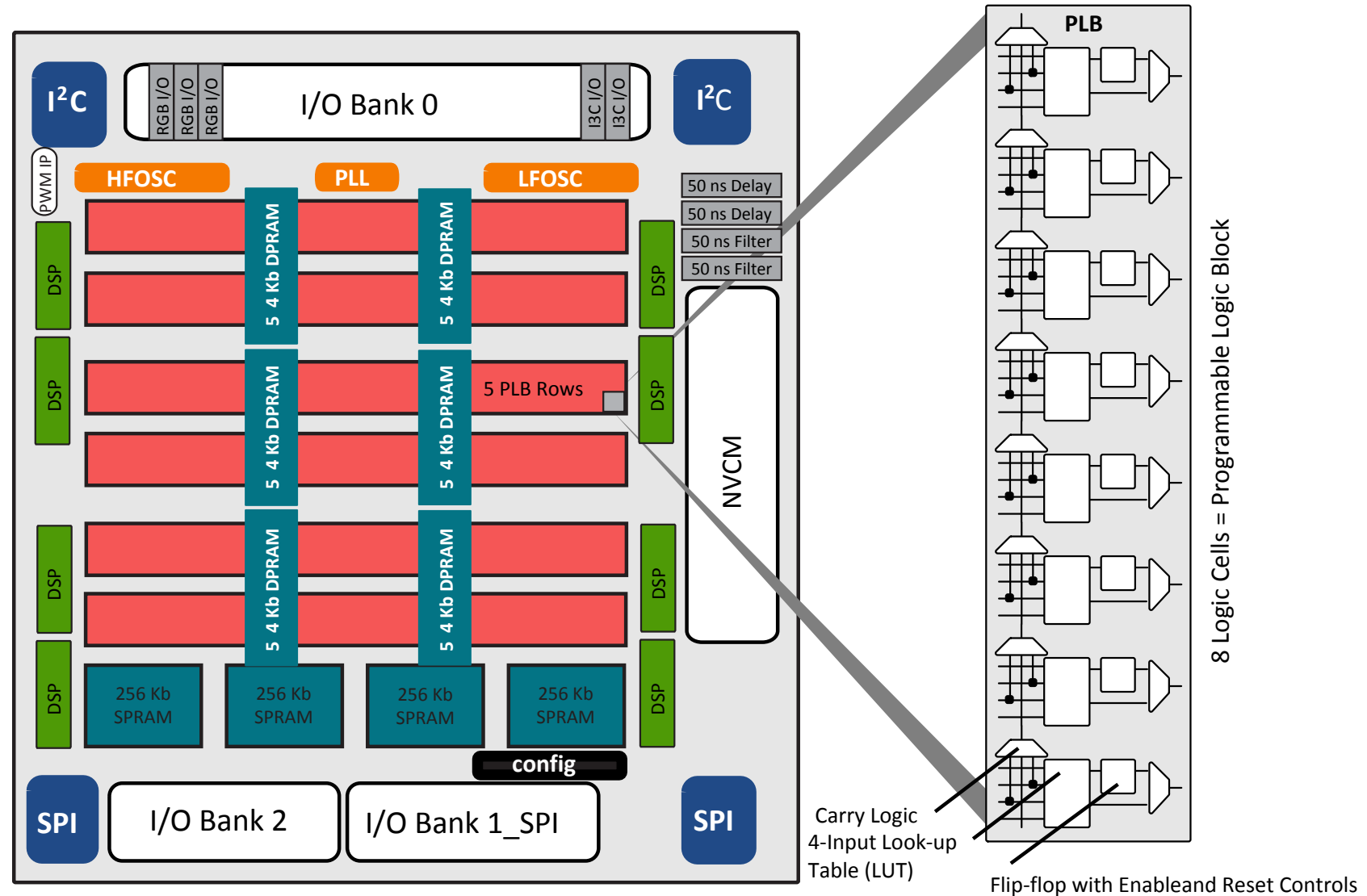


Figure 3.1. iCE40UP5K Device, Top View

iCE40UP logic element

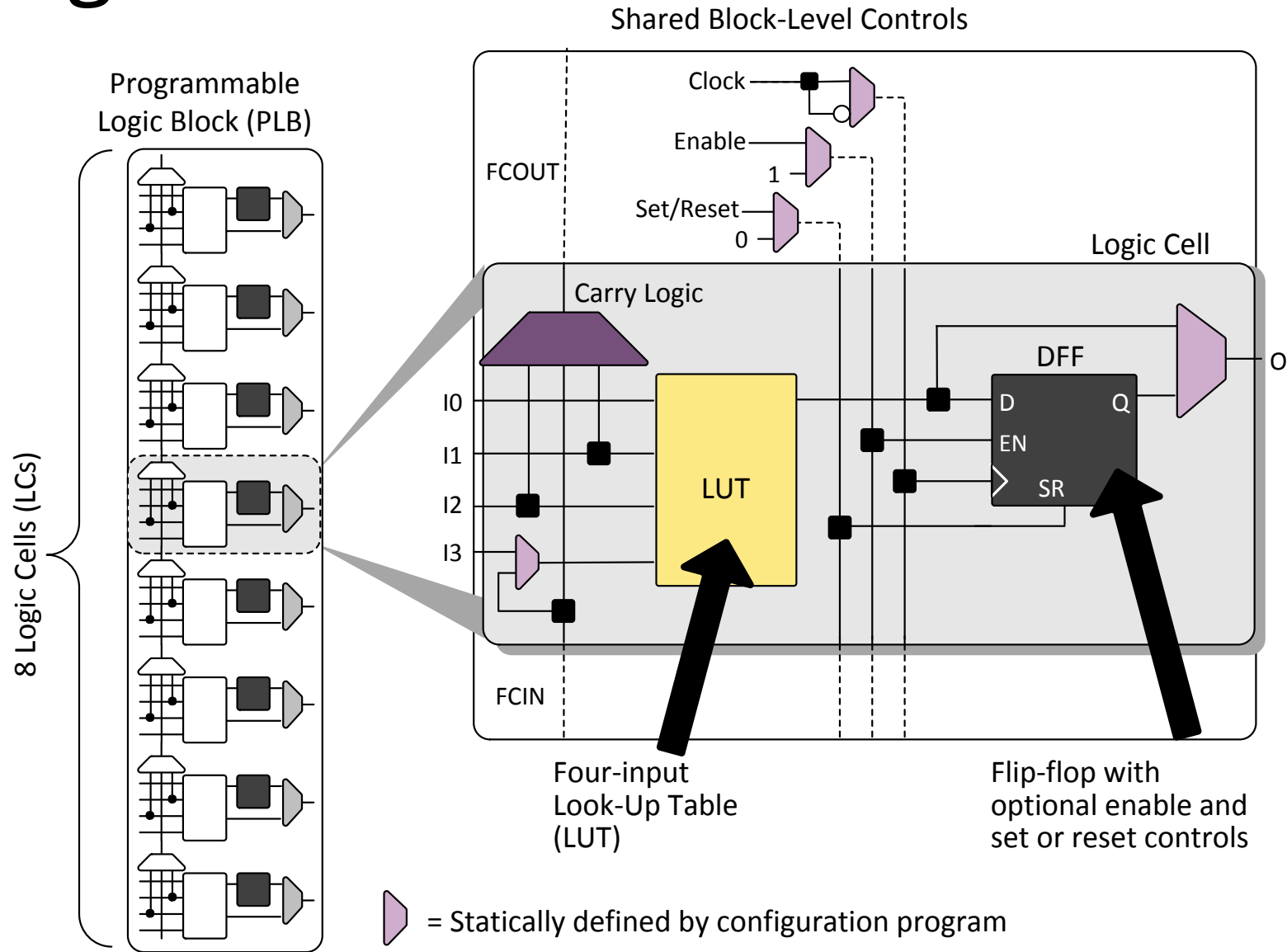


Figure 3.2. PLB Block Diagram

What is one question you have after today's class?

Respond at **pollev.com/stevenbell**

For Wednesday


1. Read the book (2.9) and complete the reading check

2. Lab 2 report is due next week at your lab time

See the video and handout (posted tonight) on the course website






3. Prelab 3 is due next week 24 hours before your lab time

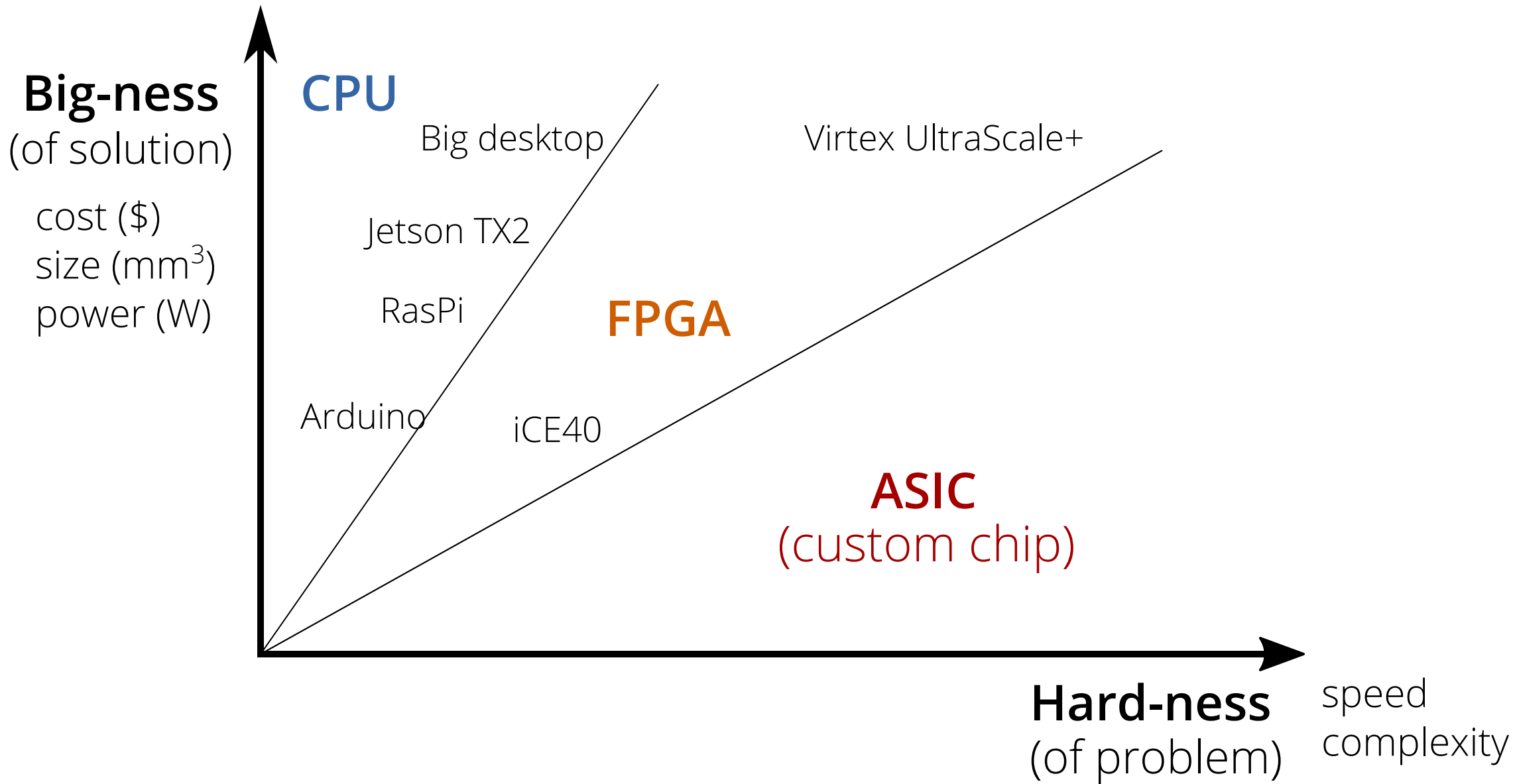4. Homework 2 (posted today) will be due next Wednesday (9/29)








Terminology

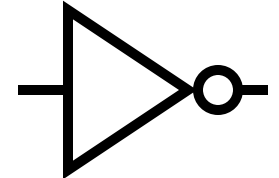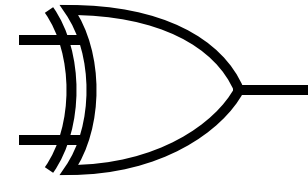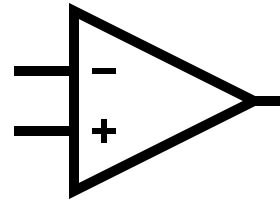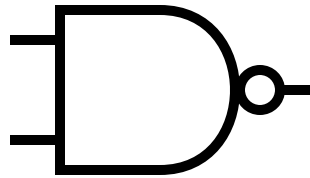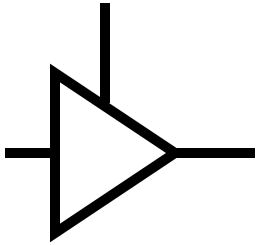Which of these is not a digital circuit element?



Terminology

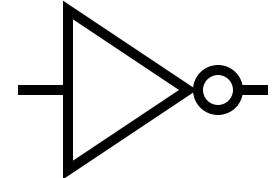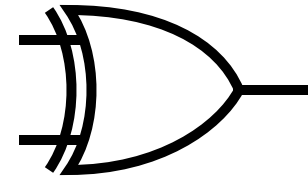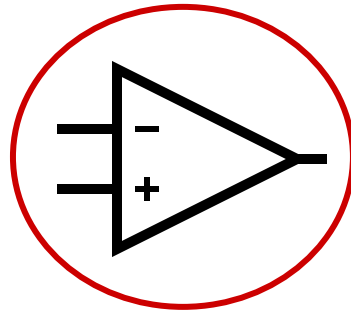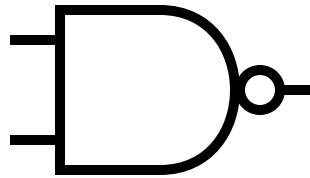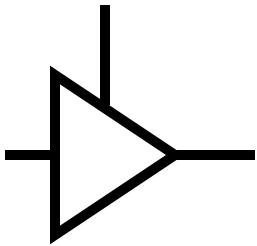Which of these is not a digital circuit element?



This is an op-amp!