

# Warmup

You are asked to organize the **Boston Marathons**, which this year will be **five separate races** on the same course.

In each race, the fastest runner will take at least **2 hours**, and the slowest runner will finish in **5 hours or less**.

Multiple races can use the course at once, but everyone from one race must finish before racers from the next race can finish.

It takes **10 minutes to reset** the finish line after the last runner crosses from each race.

**How long** will it take for all five races to finish?

Besides making people run faster, **how can you speed it up?**

# ES 4: Timing combinational logic

Steven Bell

6 February 2019

# By the end of class today, you should be able to:

- Given a circuit and timing information about the gates, calculate the contamination delay and propagation delay
- Optimize a circuit for speed
- Explain what glitches are and why they occur

# Timing

Depends on lots of things!

(excerpts from SN74LS04 datasheet)


**switching characteristics,  $V_{CC} = 5\text{ V}$ ,  $T_A = 25^\circ\text{C}$  (see Figure 1)**

PARAMETER	FROM (INPUT)	TO (OUTPUT)	TEST CONDITIONS	SN5404 SN7404			UNIT
				MIN	TYP	MAX	
$t_{PLH}$	A	Y	$R_L = 400\ \Omega$ , $C_L = 15\text{ pF}$		12	22	ns
$t_{PHL}$					8	15	

**switching characteristics,  $V_{CC} = 5\text{ V}$ ,  $T_A = 25^\circ\text{C}$  (see Figure 1)**

PARAMETER	FROM (INPUT)	TO (OUTPUT)	TEST CONDITIONS	SN54S04 SN74S04			UNIT
				MIN	TYP	MAX	
$t_{PLH}$	A	Y	$R_L = 280\ \Omega$ , $C_L = 15\text{ pF}$		3	4.5	ns
$t_{PHL}$					3	5	
$t_{PLH}$	A	Y	$R_L = 280\ \Omega$ , $C_L = 50\text{ pF}$		4.5		ns
$t_{PHL}$					5		


# Timing

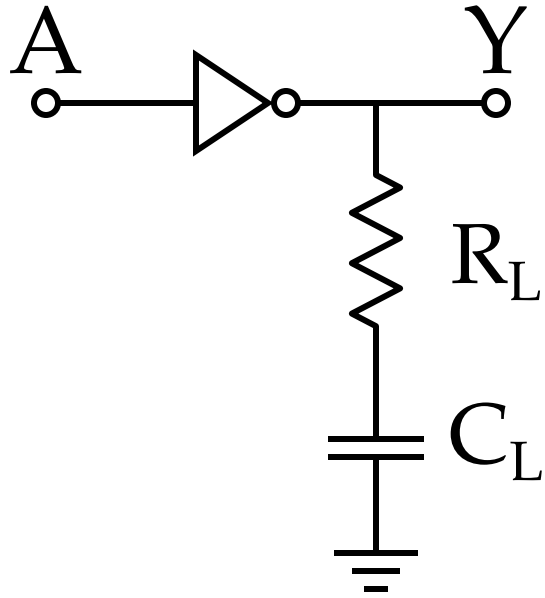
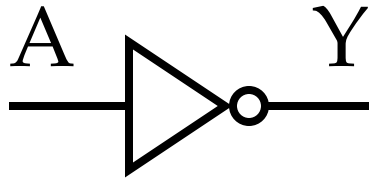
# Timing

**Contamination delay:** the soonest that the output might change


**Propagation delay:** the maximum time for the output to settle



# Timing practice

Find the contamination delay and propagation delay for this circuit


Gate	$t_{pd}$ (ps)	$t_{cd}$ (ps)
NOT	15	10
2-input NAND	20	15
3-input NAND	30	25
2-input NOR	30	25
3-input NOR	45	35
2-input AND	30	25
3-input AND	40	30
2-input OR	40	30
3-input OR	55	45
2-input XOR	60	40

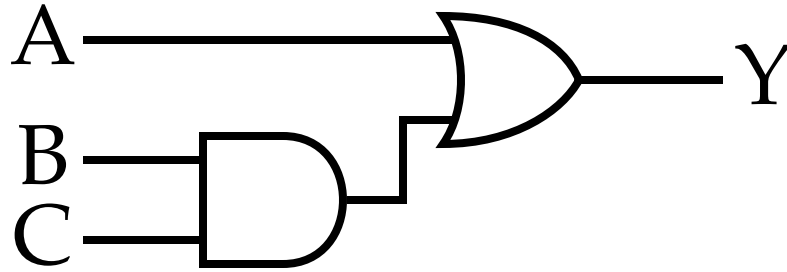
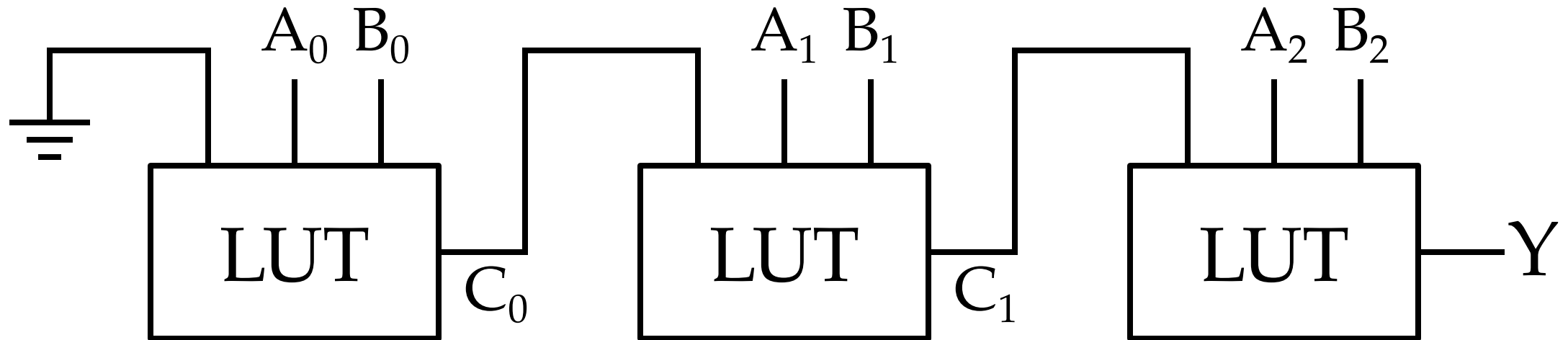
# Timing practice

Find the propagation delay for this circuit

Assume the LUT has a delay of 10ns from input (A/B) to output (C/Y)






# Who cares?

$t_{cd}$  and  $t_{pd}$  combine to determine how fast the circuit can run.

**Show and tell**

# Glitches

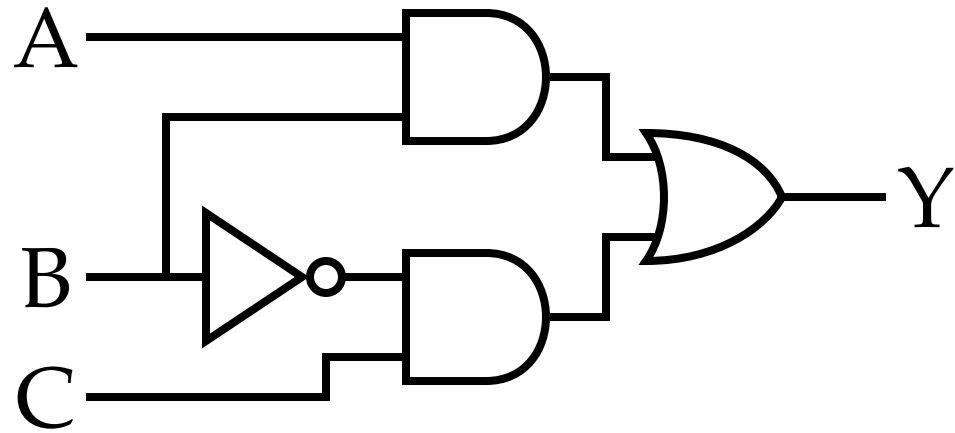

A collection of Dewalt power tools and workwear is displayed in a workshop setting. The tools, including drills, impact drivers, saws, and generators, are arranged on a metal shelving unit against a brick wall. Several tools have their lights on, creating a dramatic effect. Workwear, including jackets and a raincoat, is hanging on the wall behind the tools. The overall scene is dimly lit, with the primary light sources being the tool lights and a central text overlay.

digital design  
**POWER TOOLS!**

# For Monday

1. Read the book (4.1-4.2) and complete the pre-class quiz
2. Homework is due on Monday (2/11)
3. Lab 2 is next week; prelab due on Gradescope 24 hours in advance