

ES 4: Testing and debugging VHDL

Steven Bell

3 October 2023

By the end of class today, you should be able to:

- Explain what it means when people say code in a VHDL **process** block executes "sequentially"
- Instantiate a sub-module in VHDL
- Write a testbench for combinational logic

INTRODUCTION TO DIGITAL LOGIC

COMPUTER PROGRAMMING



VERILOG

VHDL

FIELDS OF ENLIGHTENMENT

MEMORY

PROCESS BLOCK PERILS

SEQUENTIAL LOGIC

SWAMPS OF ARCANESYNTAX

STATE MACHINES



YOU ARE HERE

FLIP-FLOP PASS



COMPUTER ARCHITECTURE

PLAINS OF COMBINATIONAL LOGIC

DESERT OF "HOW THINGS USED TO BE DONE"




What's the point of structural modeling?

(aka hierarchical modeling)

(aka component instantiation)


(aka *composition* in software-speak)

 


See the full videos on the course website, also Lab 5.

Instantiating a submodule in VHDL (entity declarations)
 
```
entity multigate is
  port (
    SignalA : in std_logic;
    SignalB : in std_logic;
    SignalC : in std_logic;
    result  : out std_logic
  );
end;
```


 
```
entity andgate is
  port (
    a : in std_logic;
    b : in std_logic;
    y : out std_logic
  );
end;
```



Instantiating a submodule in VHDL (architecture)

```
architecture synth of multigate is
entity component andgate is
    port(
        a : in std_logic;
        b : in std_logic;
        y : out std_logic
    );
end component;
signal ab : std_logic;
begin
    and1 : andgate port map(signalA, signalB, ab);
    and2 : andgate port map(ab, signalC, result);
end;
```

Inside an "architecture"
(but before "begin")

Component declaration
(because VHDL can't #include)

Instantiations

Anatomy of an instantiation

```
and1 : andgate port map(signalA, signalB, ab);
```



Instance name Module name

(like a variable
name)

(like a class
or type name)

Port mapping
(what connects to what?)

c++ *String* *message;*

  

Mapping ports explicitly by name:

```
and1 : andgate port map(a=>signalA, b=>signalB, y=>ab);
```


(Good practice when you have many ports!)

Instantiating a submodule in VHDL (architecture)

```
signal ab : std_logic;
```


```
and1 : andgate port map(signalA, signalB, ab);
```
 
```
and2 : andgate port map(ab, signalC, result);
```



Testbenches

 A testbench is an entity with no ports, and non-synthesizable code to test a submodule.



Who needs testbenches?

FPGA bugs are really hard to find compared to software bugs, because you have poor visibility.

And ASIC bugs are even worse!

Way more than half of digital design effort is in verification.

VHDL is concurrent

Within a module, all assignments happen simultaneously

VHDL is concurrent

Within a module, all assignments happen simultaneously

But we need some way to execute tests... like, sequentially.

Process block

`process` (SENSITIVITY) (We'll cover sensitivity in two weeks)

`begin`

stuff goes here

`end process;`

Process block

```
process (SENSITIVITY) (We'll cover sensitivity in two weeks)  
begin
```

```
end process;
```

Within a process block, statements execute from top to bottom (rather than "all at once").

(but don't get too excited yet)

Useful bits in a testbench

A process with no sensitivity will execute immediately and continuously

`wait` Wait forever (halt)

`wait for 5 ns`

↑ space here!

`assert CONDITION report "MESSAGE" severity SEVERITY`

`report` Print something to the console log

Practice!

On VHDLweb:

Write code to print "Hello, world!" once

Write code to print "Hello!", and "Goodbye!" 200ns later

Write code to check if $Y = 1$ (you'll need to set it yourself)

Write code to check if $Y = A$ and B

The big caveat

Inside a process:

statements are executed sequentially,

BUT

signals are not updated until time passes.

Practice: swap two ~~variables~~ signal values

Use the "testbench playground" on VHDLweb

Practice writing testbenches

VHDLweb "andgate" and "3-variable" problems

For next time

(I screwed up the deadlines)

1. Read the book (5.1-5.2) and complete the reading check (by 10/10)
2. Lab report 3 due next week, Lab 2 graded by this weekend
3. HW 2 & 3 due next week
4. Exam 1 is next Tuesday

Printing debugging info

```
report "hello, world!";  
signal a : std_logic_vector(3 downto 0);  
report "A is " & to_string(a);
```

(concatenation)  (conversion to string) 

Printing debugging info

```
report "hello, world!";  
signal a : std_logic_vector(3 downto 0);  
report "A is " & to_string(a);
```

(concatenation)  (conversion to string) 

Only in VHDL 2008!